

D.C. circuits

A-Level Physics

Practical circuits

e.m.f. and p.d.

The **electromotive force** 电动势 (e.m.f.) ε of a source is the **energy** 能量 given to each unit of charge by the source as it drives the charge around a full circuit. Unit: volt.

The **potential difference** 电势差 (p.d.) across a component is the energy changed from electrical to other forms by each unit of charge as it passes through that component.

Both are in volts; they differ in energy direction:


- e.m.f. — energy put **into** the circuit by the source (chemical $\rightarrow$ electrical in a battery, mechanical $\rightarrow$ electrical in a generator).
- p.d. — energy taken **out** of the electrical form (electrical $\rightarrow$ thermal in a resistor, $\rightarrow$ light in a lamp, $\rightarrow$ kinetic in a motor).

The examiner's wording is fixed. e.m.f. is "the energy transferred **per unit charge** by the source in driving charge round a **complete circuit**"; p.d. is "the energy transferred per unit charge from electrical to other forms". Both are energy per charge, so the volt is a joule per coulomb ($1 \text{ V} = 1 \text{ J C}^{-1}$). Statements that are **always** true of a source: the e.m.f. is the terminal p.d. when **no current** flows; the total energy it gives to a charge Q is εQ . The name is a trap: an electromotive "force" is not a force and is not measured in newtons.

Worked example. A cell of e.m.f. ε and internal resistance r drives a charge Q round a circuit whose terminal p.d. is V . Compare the energy transferred by the cell with the energy dissipated outside it.

The cell transfers εQ in total; the external circuit receives VQ . Since $V = \varepsilon - Ir < \varepsilon$ whenever a current flows, $VQ < \varepsilon Q$ — the difference $(\varepsilon - V)Q = IrQ$ is the energy turned to heat inside the cell.

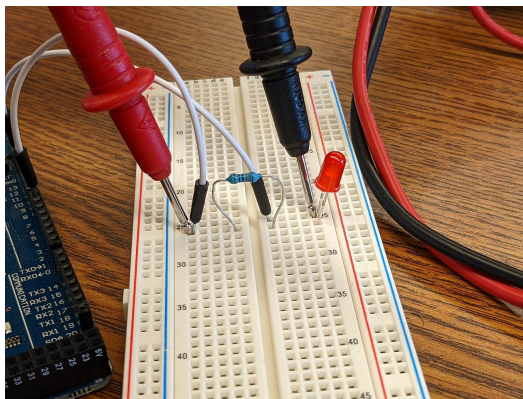In the lab you often build a circuit on a **breadboard** 面包板 (a board with rows of holes that connect components without soldering) and measure currents and p.d.s with a **multimeter** 万用表.



A real circuit on a breadboard, being measured with a multimeter

Internal resistance

A real source has some **internal resistance** 内阻 r — usually the resistance of the **electrolyte** 电解质 in a **cell** 电池, or the wire windings in a generator. When current I flows, an internal p.d. of Ir is "lost" inside the source, so the **terminal p.d.** 端电压 across the outside circuit is

$$V_{\text{terminal}} = \varepsilon - Ir.$$

So:


- **no current (open circuit)** 开路, $I = 0$): the terminal p.d. equals the e.m.f.
- **larger current**: the terminal p.d. falls.
- **short circuit** 短路 ($R_{\text{external}} \rightarrow 0$): $I = \varepsilon/r$, a large current, with all the energy turned to heat inside the source.

To measure r , change the outside resistance and plot V_{terminal} against I : the line has y -intercept ε and gradient $-r$.


Worked example. A cell of e.m.f. 1.5 V and internal resistance $0.50 \, \Omega$ is connected to a $2.5 \, \Omega$ resistor. Find the current and the terminal p.d.

The e.m.f. drives the current through both resistances: $I = \frac{\varepsilon}{R + r} = \frac{1.5}{2.5 + 0.50} = 0.50 \, \text{A}$. Then
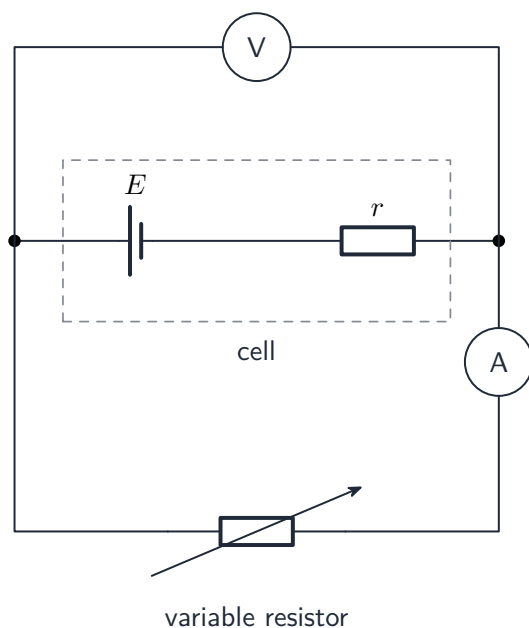
$$V_{\text{terminal}} = \varepsilon - Ir = 1.5 - 0.50 \times 0.50 = 1.25 \, \text{V}.$$



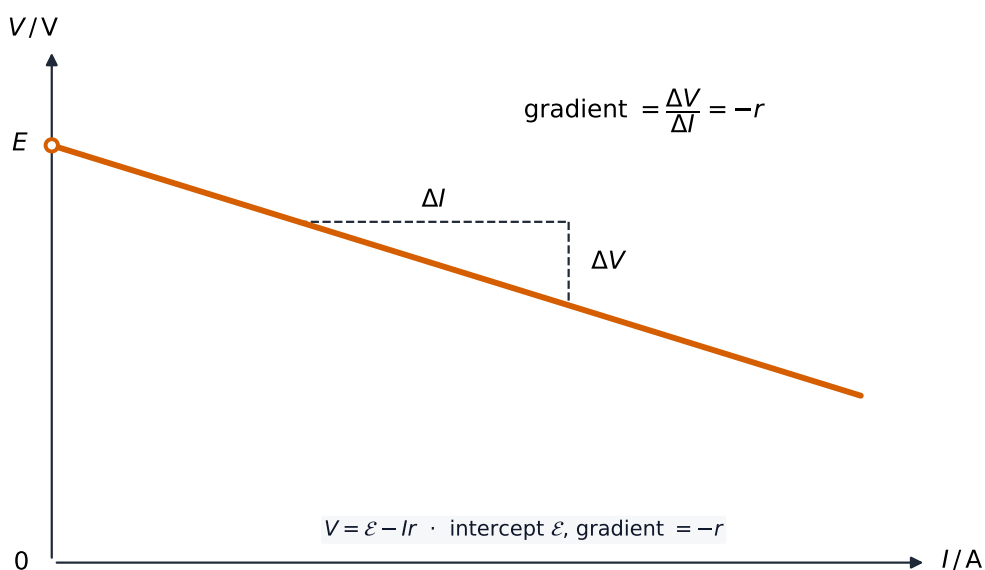Circuit for measuring the e.m.f. and internal resistance of a cell



Terminal p.d. against current — the intercept is the e.m.f. and the gradient is minus the internal resistance


The **power** 功率 given to the outside load is $P_{\text{ext}} = (\varepsilon - Ir)I$; the power lost inside is $P_{\text{int}} = I^2r$; the total power from the source is εI .

The **efficiency** 效率 of the source is $\frac{P_{\text{ext}}}{\varepsilon I} = \frac{VI}{\varepsilon I} = \frac{V}{\varepsilon} = \frac{R}{R+r}$: a large load resistance wastes little energy inside the source.

Worked example. A cell of e.m.f. 2.0 V and internal resistance 0.40 Ω drives a current of 1.5 A through a wire. Show that the terminal p.d. is 1.4 V and find the percentage efficiency with which the cell supplies power to the wire.

$V = \varepsilon - Ir = 2.0 - 1.5 \times 0.40 = 2.0 - 0.60 = 1.40$ V. Power to the wire = $VI = 1.4 \times 1.5 = 2.1$ W; total power from the cell = $\varepsilon I = 2.0 \times 1.5 = 3.0$ W. Efficiency = $2.1/3.0 = 0.70$, i.e. 70%. In a "show that" question, write every step and the unrounded value (1.40 V) before the value you were given.

When the outside circuit changes, argue through the current. Closing a switch that adds a second resistor **in parallel** lowers the total external resistance, so the current in the cell rises, the internal "lost volts" Ir rise, and the terminal p.d. $\varepsilon - Ir$ falls; the p.d. across the original resistor (which is the terminal p.d.) therefore falls, and so does its current, even though the cell's current rose. This chain — resistance $\rightarrow$ current in the cell $\rightarrow Ir \rightarrow$ terminal p.d. — is the model answer for almost every "state and explain the effect" question in this topic.

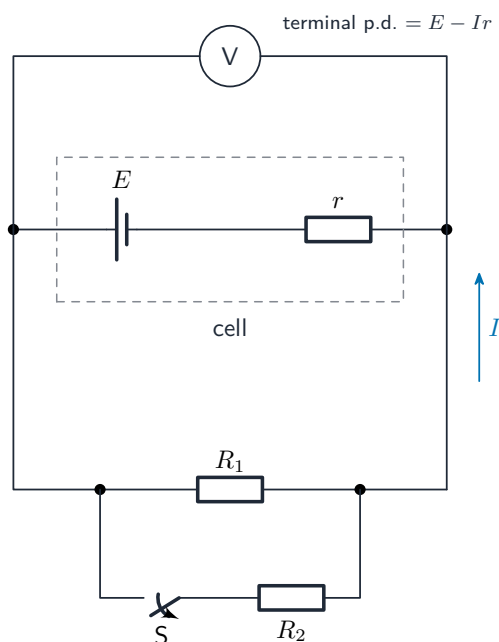


Closing S adds a parallel branch: the current in the cell rises, so Ir rises and the terminal p.d. read by the voltmeter falls

Cells joined together. In series, e.m.f.s add and internal resistances add: three cells of e.m.f. ε and internal resistance r give 3ε and $3r$. A cell connected the **wrong way round** subtracts its e.m.f. (ten 1.5 V cells with one reversed give $8 \times 1.5 = 12$ V).

Identical cells in parallel give the same e.m.f. ε with a smaller internal resistance r/N , so they can supply a larger current.


Circuit symbols

You must recognise and draw the standard symbols in the syllabus: cell, battery, switch, resistor, variable resistor, **ammeter** 电流表, **voltmeter** 电压表, lamp, **diode** (and **LED** 发光二极管), **capacitor** 电容器, inductor, thermistor, light-dependent resistor, **fuse** 保险丝, earth, junction. An ideal ammeter has zero **resistance** 电阻 and goes in **series** 串联. An ideal voltmeter has infinite resistance and goes in **parallel** 并联.

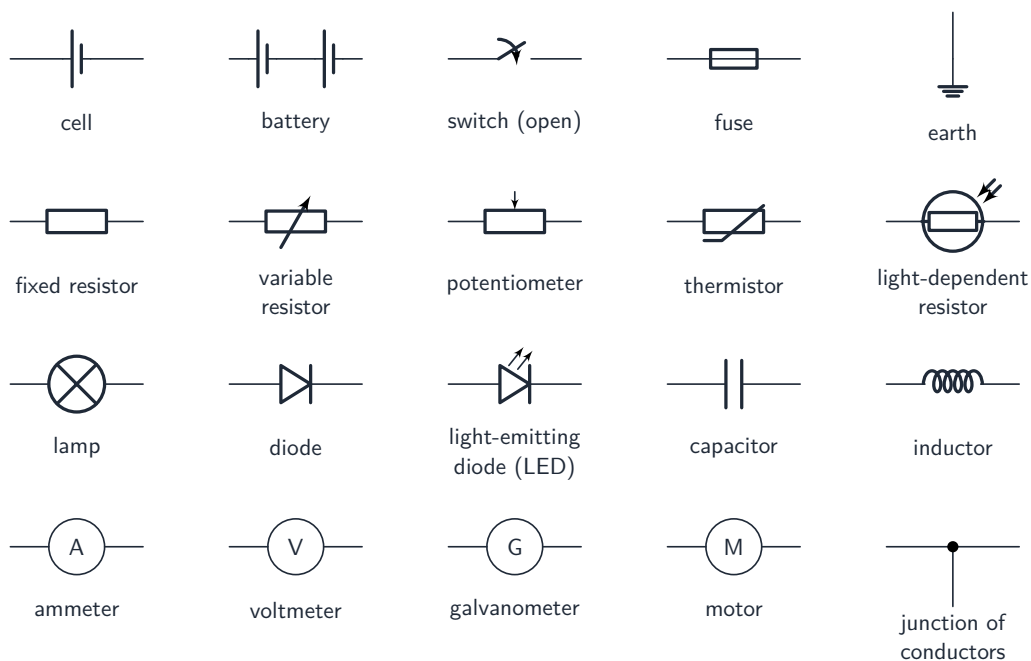


The standard circuit symbols you need to recognise and draw

Drawing a circuit diagram. Marks are lost for symbols, not physics. Use ruler-straight lines and the standard symbols; an ammeter goes **in series** with the component whose current it measures and a voltmeter **in parallel** with (across) the component whose p.d. it measures; a cell with internal resistance is drawn as an ideal cell in series with a resistor r ; and a variable resistor may be used in two ways, shown below. A "complete the circuit diagram" question usually wants exactly this measuring arrangement: source, ammeter and variable resistor in one series loop, voltmeter across the component under test.

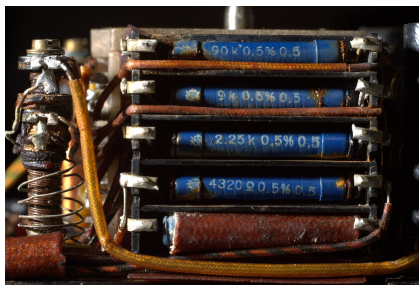

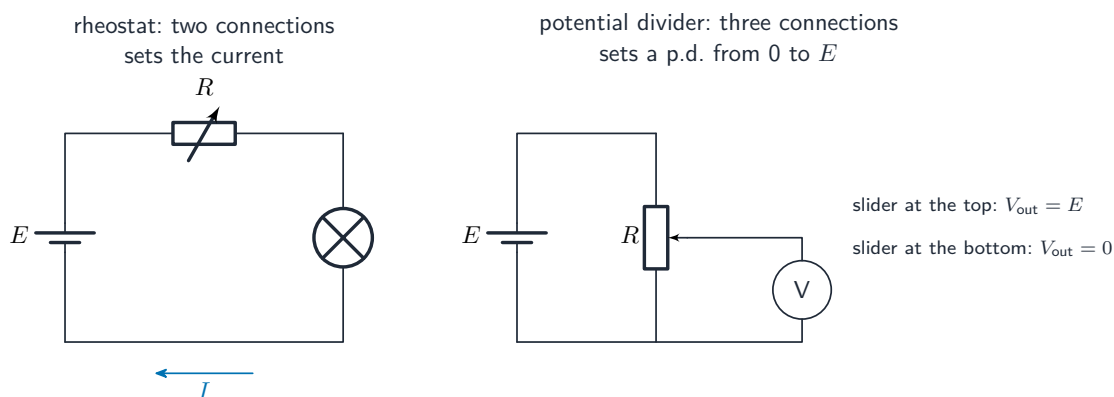A digital multimeter across a resistor bank: the voltmeter goes in parallel, the ammeter in series




A variable resistor as a rheostat (two connections, sets the current) and as a potential divider (three connections, sets a p.d. from 0 to E)

Kirchhoff's laws

First law (junction rule)

At any **junction** 节点, the **total current flowing in equals the total current flowing out**. This follows from **conservation of charge** 电荷守恒 — charge cannot build up at a point in a steady circuit, so charge in per second equals charge out per second.

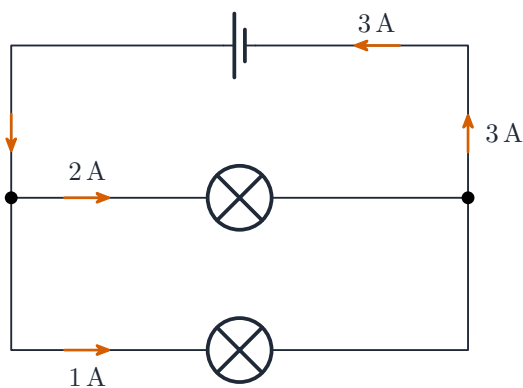For a junction with three wires: $I_1 = I_2 + I_3$ if currents 2 and 3 flow out and current 1 flows in.



at each junction: $3\text{ A} = 2\text{ A} + 1\text{ A}$

Current divides at a junction in a parallel circuit (3 A in equals 2 A plus 1 A)

Two ways the examiner asks it: “state the law” (one mark: the sum of the currents **into** a junction equals the sum of the currents **out of** it) and “state the conservation law behind it” (charge). Do not answer “energy” for the first law or “charge” for the second — the pairing is tested in almost every Paper 1.

Second law (loop rule)

Around **any closed loop** 回路, the **total e.m.f.** equals the **total p.d. across the components in that loop**. This follows from **conservation of energy** 能量守恒: as a unit of charge goes once round a loop, the energy it gains from sources equals the energy it gives up to components.

Pick a direction round the loop. Take an e.m.f. as positive when the loop direction goes from $-$ to $+$ of the source, and a p.d. as positive when the loop direction is the conventional current direction through the resistor.

In symbols, round any closed loop $\sum \varepsilon = \sum IR$. A source you pass from $+$ to $-$ counts as a **negative** e.m.f. (it is being charged, or opposes the other source), and a resistor you pass **against** its current counts as a negative p.d.

Worked example. Two batteries are in one loop with their e.m.f.s opposed: 12.0 V with internal resistance $1.0\ \Omega$, and 8.0 V with internal resistance $0.50\ \Omega$. Find the current.


Going round the loop, the net e.m.f. is $12.0 - 8.0 = 4.0\text{ V}$ and the total resistance is $1.0 + 0.50 = 1.5\ \Omega$ (the internal resistances are in series), so $I = 4.0/1.5 = 2.7\text{ A}$. The current flows in the direction driven by the larger e.m.f.

Combining resistors

Resistors in series. *Derivation using Kirchhoff's laws:* there is no junction between the resistors, so by the **first law** the same current I passes through each. By the **second law** the e.m.f. round the loop equals the sum of the p.d.s:

$$\varepsilon = IR_1 + IR_2 + \dots = I(R_1 + R_2 + \dots),$$

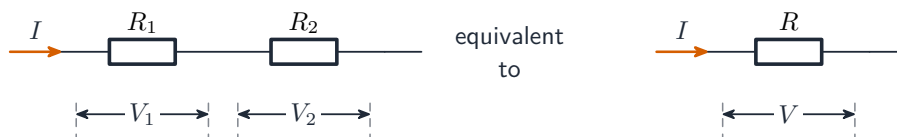so $R_{\text{series}} = R_1 + R_2 + \dots$




Two resistors in series and their single equivalent resistor

Resistors in parallel. *Derivation:* by the **second law**, each resistor forms its own loop with the source, so each has the same p.d. V across it. By the **first law** the current entering the junction equals the sum of the branch currents:

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \dots = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots \right),$$

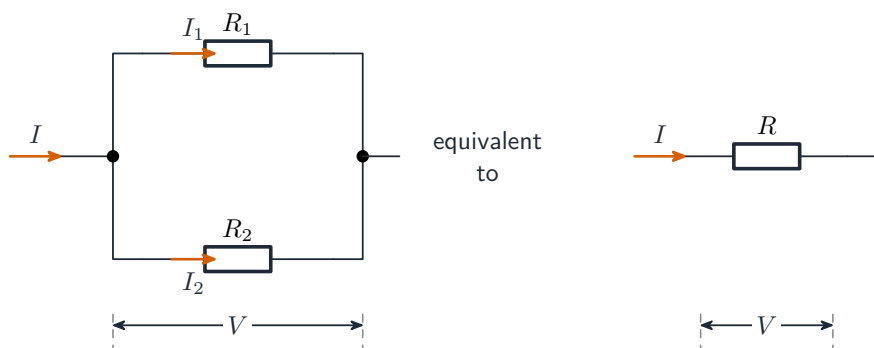so $\frac{1}{R_{\text{parallel}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$



Two resistors in parallel and their single equivalent resistor

Two equal resistors R in parallel give $R/2$; N equal ones give R/N . A parallel combination is **always smaller** than any of its resistors; a series combination is always larger.

Worked example. A $4.0\ \Omega$ resistor and a $12\ \Omega$ resistor are connected in parallel. Find their combined resistance.

$$\frac{1}{R} = \frac{1}{4.0} + \frac{1}{12} = \frac{3}{12} + \frac{1}{12} = \frac{4}{12} = \frac{1}{3} \quad \Rightarrow \quad R = 3.0\ \Omega.$$

Resistor networks and power

Reduce a mixed network **one step at a time**: replace each series chain by its sum and each parallel pair by $\frac{R_1 R_2}{R_1 + R_2}$ (the "product over sum" form, valid for two resistors only), redraw, and repeat until one resistor is left. Two rules decide **which resistor dissipates the most power** without any arithmetic: components carrying the **same current** dissipate more in the **larger** resistance ($P = I^2 R$); components with the **same p.d.** dissipate more in the **smaller** resistance ($P = V^2/R$). In a series-parallel mix the single resistor that carries the **whole** current usually dissipates the most, because a parallel branch carries only a share of it.


Worked example. Three resistors, each of resistance R , are connected with two in series and that pair in parallel with the third. The total resistance between the ends is $8.0\ \Omega$. Find R .

The series pair is $2R$; in parallel with R : $R_T = \frac{2R \times R}{2R + R} = \frac{2R}{3}$. So $\frac{2R}{3} = 8.0$, giving $R = 12\ \Omega$. Check: the single resistor R carries twice the current of the pair (same p.d., half the resistance), so it dissipates the most power.

Solving a circuit

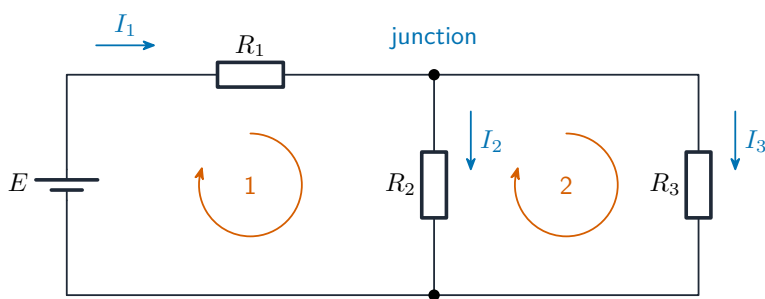1. **Label** every current with a symbol and a chosen direction.
2. **Use Kirchhoff's first law** 基尔霍夫第一定律 at each junction to link the currents.
3. **Use Kirchhoff's second law** 基尔霍夫第二定律 around each loop to get equations in the p.d.s.
4. **Use** $V = IR$ for each resistor.
5. Solve the equations together.

For symmetric resistor networks, use the symmetry to spot branches with equal currents — the branch with the most current gives the most power ($P = I^2 R$).



The standard two-loop circuit: one junction equation and two loop equations fix all three currents

Worked example. In the circuit above $\varepsilon = 12 \text{ V}$ (negligible internal resistance), $R_1 = 2.0 \, \Omega$, $R_2 = 6.0 \, \Omega$ and $R_3 = 3.0 \, \Omega$. Find the three currents.

Kirchhoff's method. Junction: $I_1 = I_2 + I_3$. Loop 1 (through ε , R_1 , R_2): $12 = 2.0I_1 + 6.0I_2$. Loop 2 (through R_2 and R_3 , no source): $0 = 6.0I_2 - 3.0I_3$, so $I_3 = 2I_2$. Then $I_1 = 3I_2$ and $12 = 6.0I_2 + 6.0I_2$, giving $I_2 = 1.0 \text{ A}$, $I_3 = 2.0 \text{ A}$ and $I_1 = 3.0 \text{ A}$.

Reduction check. $6.0 \, \Omega$ and $3.0 \, \Omega$ in parallel give $2.0 \, \Omega$; with R_1 the total is $4.0 \, \Omega$, so $I_1 = 12/4.0 = 3.0 \text{ A}$ and the p.d. across the parallel pair is $3.0 \times 2.0 = 6.0 \text{ V}$, giving $I_2 = 6.0/6.0 = 1.0 \text{ A}$ and $I_3 = 6.0/3.0 = 2.0 \text{ A}$. Both methods must agree; a negative answer for a current simply means you guessed its direction the wrong way.

Potential dividers

A **potential divider** 分压器 is two (or more) resistors in series across a source. The p.d. across each resistor is in **direct proportion** to its resistance:


$$V_1 = V_{\text{in}} \cdot \frac{R_1}{R_1 + R_2}, \quad V_2 = V_{\text{in}} \cdot \frac{R_2}{R_1 + R_2}.$$

The output (tapped between R_1 and R_2) can be set to any **voltage** 电压 between 0 and V_{in} by choosing the resistances. A **potentiometer** 电位差计 used with all three of its connections (a slider on a uniform-resistance track) gives a smoothly variable divider; the same component with only two connections is a **rheostat** 变阻器, which just changes the current.

Worked example. A 6.0 V supply is connected across a $2.0 \text{ k}\Omega$ resistor in series with a $4.0 \text{ k}\Omega$ resistor. Find the output voltage tapped across the $4.0 \text{ k}\Omega$ resistor.

$$V_2 = V_{\text{in}} \cdot \frac{R_2}{R_1 + R_2} = 6.0 \times \frac{4.0}{2.0 + 4.0} = 4.0 \text{ V}.$$

The same answer comes from the **current-first** route the mark scheme often lays out: $I = V_{\text{in}}/(R_1 + R_2) = 6.0/6000 = 1.0 \text{ mA}$, then $V_2 = IR_2 = 1.0 \times 10^{-3} \times 4000 = 4.0 \text{ V}$. Two consequences worth remembering: the **larger** resistance takes the **larger** share of the p.d.; and the ratio formula holds only while **no current is drawn from the output** — a load (or a low-resistance voltmeter) in parallel with R_2 lowers the effective resistance of R_2 and so lowers V_2 .

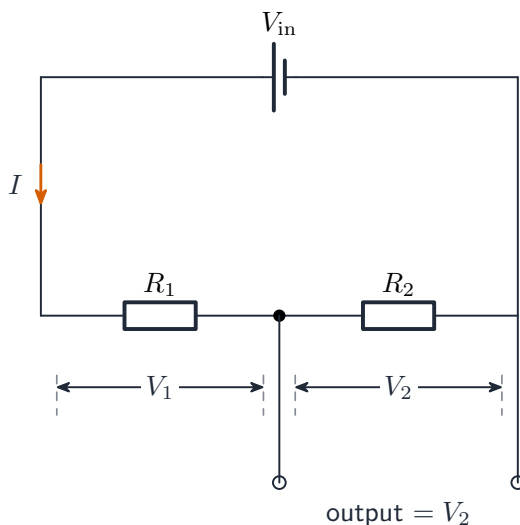


A potential divider — the p.d. splits between R_1 and R_2 in proportion to their resistances

Sensor circuits

Replace one fixed resistor with a **sensor** 传感器 whose resistance changes with a physical quantity:

- **thermistor** 热敏电阻 (NTC): R falls as temperature rises. In a divider, the output voltage changes with temperature in a fixed direction.
- **light-dependent resistor** 光敏电阻 (LDR): R falls as **light intensity** 光强 rises, giving a brightness-dependent output.

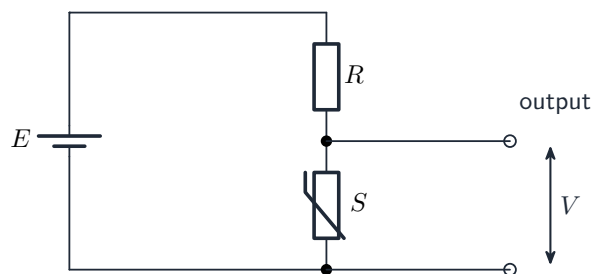Connect the output to a **transistor** 晶体管 base or a **comparator** 比较器 to switch a load on or off when the temperature or light passes a **threshold** 阈值.




A thermistor in a potential divider gives an output voltage that changes with temperature


Which way does the output go? The output can be taken across the **sensor** or across the **fixed resistor**, and the two choices respond in opposite directions. Argue through the current, in this order, and you have the full three-mark answer:

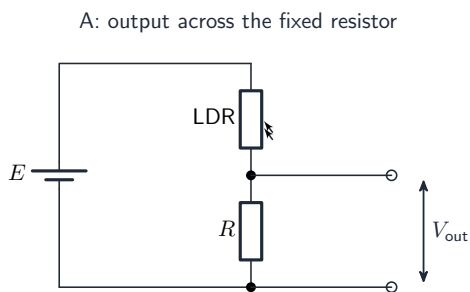1. the light gets brighter (or the temperature rises), so the resistance of the LDR (or thermistor) **falls**;
2. the total resistance of the series circuit falls, so the **current rises** ($I = \varepsilon / R_{\text{total}}$);
3. the p.d. across the **fixed resistor** = IR **rises**, so the p.d. across the **sensor** = $\varepsilon - IR$ **falls**.

So an output across the fixed resistor **rises** with light or temperature; an output across the sensor **falls**. If the source has internal resistance, add one more link: the larger current also increases Ir , so the terminal p.d. falls slightly.



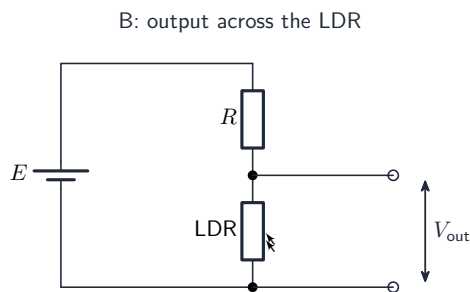brighter light $\Rightarrow V_{\text{out}}$ rises



brighter light $\Rightarrow V_{\text{out}}$ falls

Where you take the output decides the direction of the change: across the fixed resistor it rises with light, across the LDR it falls

Worked example. A battery of e.m.f. 9.0 V and negligible internal resistance is connected in series with an LDR and a $1200\ \Omega$ resistor. In the light the LDR has a resistance of $1800\ \Omega$. Calculate the p.d. across the LDR, and state and explain what happens to it when the light intensity decreases.

$V_{\text{LDR}} = 9.0 \times \frac{1800}{1800 + 1200} = 5.4 \text{ V}$. Less light $\rightarrow$ the resistance of the LDR increases $\rightarrow$ the total resistance increases and the current **decreases** $\rightarrow$ the p.d. across the 1200Ω resistor (IR) decreases $\rightarrow$ the p.d. across the LDR ($9.0 - IR$) **increases**.

Worked example. A thermistor in series with a 5800Ω resistor across a 6.0 V supply gives a p.d. of 2.9 V across the resistor. Find the resistance of the thermistor.

Current $= 2.9/5800 = 5.0 \times 10^{-4} \text{ A}$. The thermistor takes the remaining $6.0 - 2.9 = 3.1 \text{ V}$, so $R = 3.1/(5.0 \times 10^{-4}) = 6200 \Omega$ (or, by ratio, $R = 5800 \times 3.1/2.9$).

Potentiometer and the null method


A **potentiometer** is a uniform resistance wire of length L_0 with a sliding contact (**jockey** 滑动触头). The resistance per unit length is uniform, so the p.d. from one end to the jockey is proportional to the length:

$$V_x = V_{\text{full}} \cdot \frac{x}{L_0}.$$

To **compare two e.m.f.s** (an unknown cell against a standard cell), connect each in turn with the jockey through a **galvanometer** 检流计. Slide the jockey until the galvanometer reads zero (a **null** — no current flows through the cell being measured, because the potentiometer's voltage there exactly opposes the cell's e.m.f.). The **balance length** 平衡长度 — the wire length from the end to the jockey at balance — is proportional to the e.m.f. being measured, so the two lengths are in the ratio of the e.m.f.s:

$$\frac{\varepsilon_1}{\varepsilon_2} = \frac{l_1}{l_2}.$$

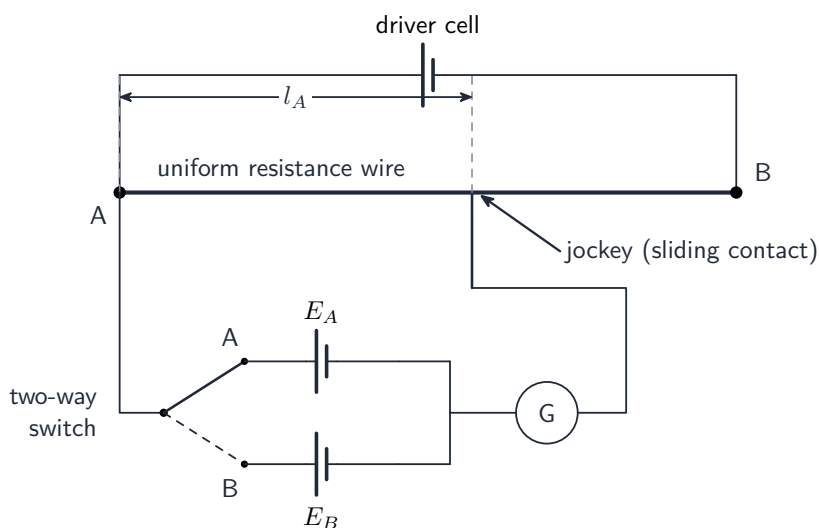This is a **null method** 零点法: you find the balance (zero current) instead of measuring a current's value. Its advantage is that at balance the unknown cell gives no current, so its internal resistance does not affect the result.



A potentiometer comparing two cell e.m.f.s by the null method

Why the null method is better than a voltmeter. At balance no current is drawn from the cell being measured, so there is no Ir drop inside it: the balance point measures the **e.m.f.**, not the terminal p.d. A voltmeter always draws some current, so it reads slightly less than the e.m.f.

Reading the balance point. The p.d. per unit length of the wire is fixed by the **driver cell** 驱动电池 and the resistance of the wire. Anything that makes the p.d. being balanced **larger** moves the balance point **further** along the wire; anything that makes the p.d. per unit length larger (a driver cell of larger e.m.f., or a wire that takes a larger share of the driver's p.d.) makes the balance length **shorter**. Replacing the wire by one of the same length but **greater diameter** lowers its resistance ($R = \rho L/A$): if the driver cell has negligible internal resistance and nothing else is in series, the p.d. across the wire is still the full e.m.f. and the balance length does not move; if the driver has internal resistance or a series resistor, the wire's share of the e.m.f. falls, the p.d. per metre falls, and the balance length grows. Say which case you are in.

Worked example. A potentiometer wire XY of length 2.0 m carries a p.d. of 1.50 V. A cell of e.m.f. E is balanced when the jockey is 1.6 m from X. Find E , and state what happens to the balance length if the driver cell is replaced by one of larger e.m.f.

$E = 1.50 \times \frac{1.6}{2.0} = 1.2 \text{ V}$. A larger driver e.m.f. gives a larger p.d. per metre, so the same 1.2 V is reached at a **shorter** length: the jockey must move towards X.

Definitions the examiner accepts

A definition question is marked against fixed wording. Learn these exactly, and give one answer only.

Term	Definition
electromotive force (e.m.f.)	the energy transferred per unit charge by a source in driving charge round a complete circuit
potential difference (p.d.)	the energy transferred per unit charge from electrical energy to other forms of energy
internal resistance	the resistance to current inside a source of e.m.f., which causes a p.d. Ir across the source when a current flows
terminal p.d.	the p.d. across the terminals of a source, equal to e.m.f. $-Ir$
Kirchhoff's first law	the sum of the currents into a junction is equal to the sum of the currents out of the junction (conservation of charge)
Kirchhoff's second law	the sum of the e.m.f.s round a closed loop is equal to the sum of the p.d.s round the loop (conservation of energy)
potential divider	two or more resistors in series across a supply, giving a p.d. across one of them that is a fraction of the supply p.d.
potentiometer	a uniform resistance wire with a sliding contact, used to compare p.d.s by finding the length at which a galvanometer reads zero
null method	a measurement made by adjusting a circuit until a meter reads zero, so no current is drawn from the component being measured
balance length	the length of potentiometer wire between one end and the sliding contact when the galvanometer reads zero

Exam tips

- Apply **Kirchhoff's laws**: current into a junction = current out (charge conserved); $\sum \text{e.m.f.} = \sum \text{p.d.}$ round a loop (energy conserved). Name the law you are using when a question says "use Kirchhoff's laws".
- Combine resistors: **series** $R = R_1 + R_2$; parallel $1/R = 1/R_1 + 1/R_2$. A parallel combination is always smaller than its smallest resistor.

- A **potential divider** splits voltage in the ratio of the resistances; the larger resistance takes the larger p.d.
- Include **internal resistance**: $\text{e.m.f.} = I(R + r)$ — the "lost volts" are Ir . When a circuit changes, argue resistance $\rightarrow$ current in the cell $\rightarrow Ir \rightarrow$ terminal p.d.
- "Negligible internal resistance" means the terminal p.d. **is** the e.m.f., whatever the current. Look for the phrase before you start.
- Read a V - I graph of a source as $V = \varepsilon - Ir$: intercept ε , gradient $-r$, and the current at $V = 0$ is the maximum (short-circuit) current ε/r .
- In Paper 5, rearrange the circuit relation into $y = mx + c$ before plotting: a cell of e.m.f. ε and internal resistance r feeding n equal resistors R in parallel obeys $\varepsilon = I \left(\frac{R}{n} + r \right)$, so $\frac{1}{I} = \frac{R}{\varepsilon} \cdot \frac{1}{n} + \frac{r}{\varepsilon}$ — a graph of $1/I$ against $1/n$ has gradient R/ε and intercept r/ε .

Common mistakes

- Writing $V = IR$ with the e.m.f. and the external resistance only, forgetting r . Use $\varepsilon = I(R + r)$.
- Saying e.m.f. is "the force that pushes the charge". It is energy per unit charge; the volt is a joule per coulomb.
- Pairing the laws with the wrong conservation law. First law — charge; second law — energy.
- Using "product over sum" for three parallel resistors. It works for two only; otherwise add the reciprocals.
- Explaining a sensor circuit by "the resistance changes so the voltage changes". The marks are for the chain: resistance $\rightarrow$ total resistance $\rightarrow$ current $\rightarrow IR$ across the fixed resistor $\rightarrow$ the rest across the sensor.
- Claiming a potentiometer at balance "draws no current from the driver cell". It draws none from the **cell being measured**; the driver cell always supplies the wire current.
- Rounding a "show that" value before the last line — write 1.40 V, then say it is 1.4 V.