

Exercise walk-through

Capacitors and capacitance ■ 19.1

eXercise


You must be able to

- define **capacitance** and use $C = Q/V$
- combine capacitors in **series** and **parallel**


Method — Capacitance

A **capacitor** stores charge: $+Q$ on one plate, $-Q$ on the other, with p.d. V across the gap:
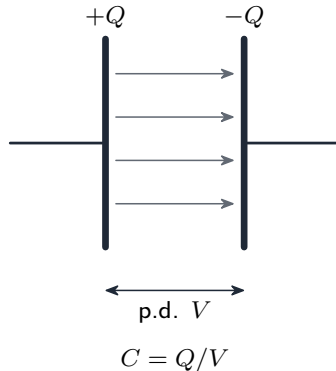
$$C = \frac{Q}{V} \quad (\text{farad, } F = C \text{ V}^{-1}).$$



Method — Capacitance

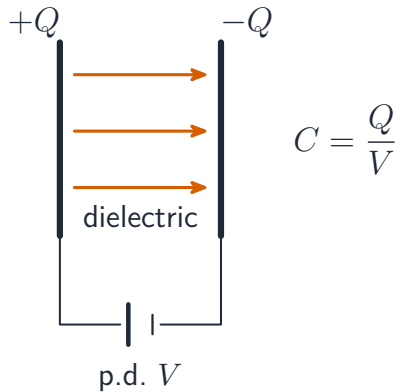

A parallel-plate capacitor

Method — Combining capacitors (opposite to resistors)

■ **parallel:** $C = C_1 + C_2 + \dots$

■ **series:** $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$

Practice 2.1 ■ 1 mark

Define **capacitance**.

Solution 2.1

Method: Capacitance

Worked steps

The **charge stored per unit potential difference** ($C = Q/V$) **B1**.

Practice 2.2 ■ 1 mark

State the **unit** of capacitance.

Solution 2.2

Method: Capacitance

Worked steps

The **farad** (F) **B1**.

Practice 2.3 ■ 2 marks

A capacitor holds $60\ \mu\text{C}$ of charge at $12\ \text{V}$. Find its **capacitance**.

Solution 2.3

Method: Capacitance

Worked steps

$$C = Q/V = (60 \times 10^{-6})/12 = 5.0 \mu\text{F} \quad \text{M1} \quad \text{A1}.$$

Practice 2.4 ■ 1 mark

Write the formula for capacitors in **parallel**.

Solution 2.4

Worked steps

$$C = C_1 + C_2 + \dots \quad \text{B1}.$$

Exam-style 3.1 ■ 1 mark

The unit of capacitance is the:

A coulomb

B farad

C volt

D ohm

Solution 3.1

Method: Capacitance

A coulomb

B farad



C volt

D ohm

Worked steps

B — farad.

Exam-style 3.2 ■ 2 marks

A $100\ \mu\text{F}$ capacitor is charged to $9.0\ \text{V}$. Calculate the **charge** stored.

Solution 3.2

Method: Capacitance

Worked steps

$$Q = CV = (100 \times 10^{-6})(9.0) = 9.0 \times 10^{-4} \text{ C} \quad \text{M1} \quad \text{A1}.$$

Exam-style 3.3 ■ 3 marks

A $4.0\ \mu\text{F}$ and a $2.0\ \mu\text{F}$ capacitor are connected in **series**. Calculate the combined capacitance.

Solution 3.3

Method: Capacitance

Worked steps

$$\frac{1}{C} = \frac{1}{4.0} + \frac{1}{2.0} = \frac{3}{4.0} \quad \text{M1 M1}; C = 1.3 \mu\text{F} \quad \text{A1}.$$

Exam-style 3.4 ■ 1 mark

Write the formula for capacitors in **series**.

Solution 3.4

Method: Combining capacitors (opposite to resistors)

Worked steps

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \dots \quad \text{B1}.$$

Exam-style 3.5 ■ 2 marks

Three capacitors are available: $C_1 = 120 \mu\text{F}$, $C_2 = 180 \mu\text{F}$ and $C_3 = 220 \mu\text{F}$.

(a) C_1 and C_2 are connected in **series** across a supply. **Complete** the table to show how the charge on each and the p.d. across each relate to the total charge Q_S and the supply p.d. V_S .

quantity	relationship
charges Q_1 , Q_2 and Q_S	_____
p.d.s V_1 , V_2 and V_S	_____

Exam-style 3.5 ■ 2 marks

- (b) **Determine** the combined capacitance of C_1 and C_2 in series.
- (c) The supply provides 12 V. **Calculate** the charge stored by that series combination, and the p.d. across C_1 .
- (d) C_3 is now connected in **parallel** with the series pair. **Determine** the total capacitance of the whole network, and the total charge it now stores at 12 V.
- (e) **State and explain** which single capacitor in the network stores the **most** charge.

Solution 3.5

Method: Capacitance

Worked steps

(a) Charges: $Q_1 = Q_2 = Q_S$ — the same charge passes through every capacitor in a series chain **B1**. P.d.s: $V_1 + V_2 = V_S$ **B1**.

(b) $\frac{1}{C} = \frac{1}{120} + \frac{1}{180}$ **M1**, so $C = \frac{120 \times 180}{300} = 72 \mu\text{F}$ **A1**.

(c) $Q = CV = 72 \times 10^{-6} \times 12 = 8.6 \times 10^{-4} \text{ C}$ **M1 A1**;

$V_1 = \frac{Q}{C_1} = \frac{8.64 \times 10^{-4}}{120 \times 10^{-6}} = 7.2 \text{ V}$ **A1**. (The **smaller** capacitor takes the larger share of the p.d.)

(d) Capacitors in parallel add: $C_{\text{total}} = 72 + 220 = 292 \mu\text{F}$ **M1 A1**;

Solution 3.5

$$Q_{\text{total}} = 292 \times 10^{-6} \times 12 = 3.5 \times 10^{-3} \text{ C} \quad \text{A1}.$$

(e) C_3 **B1** — it has the full 12 V across it and the largest capacitance, so $Q = CV$ is largest; the series pair shares the same p.d. between two capacitors and behaves as only $72 \mu\text{F}$ **B1**.