

Past-paper walk-through

Energy stored in a capacitor ■ 19.2

eXercise

Questions in this set

- 9702/41 N25 Q6 ■ 11 marks
- 9702/42 M24 Q4 ■ 10 marks
- 9702/42 M23 Q5 ■ 10 marks

Reading the mark scheme

- **B1** a mark that stands on its own – the point is either made or not.
- **M1** a *method* mark: the right approach, even if the number is wrong.
- **A1** an *answer* mark, and it usually needs its M mark first.
- **C1** a working mark on the way to the answer.
- **//** separates answers the examiner accepts equally.
- **ecf** = error carried forward: a later part is marked on your own earlier answer.
- **owtte** = “or words to that effect” – the wording need not match.

Question 6

9702/41 N25 ■ Q6 ■ 11 marks

Two parallel plate capacitors C_1 and C_2 are connected to a supply that has a potential difference (p.d.) V_S . The capacitors may be connected in series or in parallel.

The supply provides charge Q_S and the plates of the two capacitors acquire charges Q_1 and Q_2 respectively. The p.d.s across the plates of the capacitors are V_1 and V_2 respectively.

(a) Complete Table 6.1 to indicate how Q_S , Q_1 and Q_2 relate to each other, and how V_S , V_1 and V_2 relate to each other, for series and parallel connections of the capacitors to the supply.

Table 6.1

	relationship between charges	relationship between p.d.s
series		
parallel		

Question 6

[4]

Question 6

	relationship between charges	relationship between p.d.s
series		
parallel		

Question 6

9702/41 N25 ■ Q6 ■ 11 marks

Two parallel plate capacitors C_1 and C_2 are connected to a supply that has a potential difference (p.d.) V_S . The capacitors may be connected in series or in parallel.

The supply provides charge Q_S and the plates of the two capacitors acquire charges Q_1 and Q_2 respectively. The p.d.s across the plates of the capacitors are V_1 and V_2 respectively.

(b)(i) Calculate the p.d. across the capacitor. [2]

(b)(ii) Calculate the charge on the capacitor. [2]

(b)(iii) The capacitor is now connected in parallel with a capacitor of capacitance $180\ \mu\text{F}$ that is initially uncharged.

Determine the total energy, in mJ, now stored in the two capacitors. [3]

Solution 6

(a) Mark scheme

- series charges:
- $Q_S = Q_1 = Q_2$ (B1)
- series p.d.s:
- $V_S = V_1 + V_2$ (B1)
- parallel charges: $Q_S = Q_1 + Q_2$ (B1)
- parallel p.d.s:
- $V_S = V_1 = V_2$ (B1)

Solution 6

(b)(i) Worked steps

- $E = \frac{1}{2}CV^2$, so $V = \sqrt{\frac{2E}{C}}$.

- $V = \sqrt{\frac{2 \times 19 \times 10^{-3}}{470 \times 10^{-6}}}$

- $V = 9.0 \text{ V}$

Solution 6

Mark scheme

- $E = \frac{1}{2} CV^2$ (C1)
- $\text{p.d.} = [(2 \times 19 \times 10^{-3}) / (470 \times 10^{-6})]^{1/2}$
- $= 9.0 \text{ V}$ (A1)

Solution 6

(b)(ii)

Worked steps

Now that the p.d. is known, the charge follows from the definition of capacitance.

- $Q = CV = 470 \times 10^{-6} \times 9.0$
- $Q = 4.2 \times 10^{-3} \text{ C}$

Or in one step from the energy: $Q = \sqrt{2EC}$, which avoids carrying a rounded V .

Mark scheme

- $E = Q^2 / 2C$ or $C = Q / V$ **C1**
- $Q = (19 \times 10^{-3} \times 2 \times 470 \times 10^{-6})^{1/2}$ or
- $Q = 470 \times 10^{-6} \times 9.0$
- $Q = 4.2 \times 10^{-3} \text{ C}$ **A1**

Solution 6

(b)(iii) Worked steps

Connecting a second capacitor in **parallel** to a charged one shares the charge, and the total charge is conserved.

- Total capacitance: $C = (470 + 180) \times 10^{-6} = 650 \mu\text{F}$.
- The charge is unchanged at $Q = 4.2 \times 10^{-3} \text{ C}$ from part (b)(ii).
- $E = \frac{Q^2}{2C} = \frac{(4.23 \times 10^{-3})^2}{2 \times 650 \times 10^{-6}}$
- $E = 0.014 \text{ J} = 14 \text{ mJ}$

Solution 6

Energy fell from 19 mJ to 14 mJ even though no charge was lost — the missing 5 mJ is dissipated in the connecting wires as the charge redistributes, which is the point the question is testing.

Mark scheme

- total charge unchanged **C1**
- total capacitance = $(470 + 180) \times 10^{-6}$ (F) **C1**
- $E = Q^2 / 2C = (4.23 \times 10^{-3})^2 / (2 \times 650 \times 10^{-6})$ (= 0.014 J)
- $E = 14$ mJ **A1**

Question 4

9702/42 M24 ■ Q4 ■ 10 marks

Three capacitors are connected as shown in Fig. 4.1.

(a) Determine the total capacitance, in μF , of the network of three capacitors. [2]

(b) A capacitor of capacitance $45 \mu\text{F}$ is connected to a variable power supply initially set at 8.0V . The output of the power supply increases so that the potential difference (p.d.) across the capacitor increases to 9.6V .

Calculate the increase in energy ΔE stored in the capacitor. [2]

(c)(i) Complete the circuit in Fig. 4.2 by adding a capacitor to smooth the p.d. across the load resistor. [1]

(c)(ii) The variation with time t of the p.d. V of the smoothed output is shown in Fig. 4.3.

Determine the time constant, in ms, of the smoothing circuit. [3]


(d)(i) full-wave rectified [1]

Question 4

(d)(ii) half-wave rectified.

[1]

Question 4

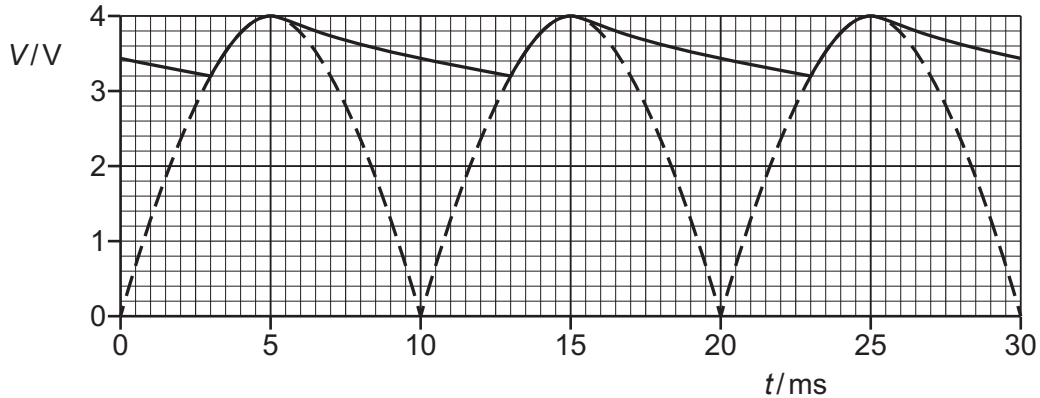

Solution 4

(a) Worked steps

Know. Work outwards from the inside of the network. Capacitors in **parallel** add directly; capacitors in **series** add as reciprocals. The rules are the opposite way round to resistors, which is where most marks are lost.

Parallel pair. The two parallel capacitors combine to $15 + 15 = 30 \mu\text{F}$.

In series with the third. $\frac{1}{C} = \frac{1}{45} + \frac{1}{30}$.

Solution 4

Answer. $C = \left(\frac{1}{45} + \frac{1}{30} \right)^{-1} = 18 \mu\text{F}.$

Check. A series combination must be **smaller** than either capacitor in it, and $18 < 30$, so the answer is the right side of both. Forgetting the final reciprocal leaves 0.056, an obvious flag.

Mark scheme

- combined capacitance of parallel capacitors = $30 (\mu\text{F})$
- total capacitance = $(1/45 + 1/30)^{-1}$
- = $18 \mu\text{F}$

Solution 4

(b) Worked steps

Know. “Increase in energy” means the difference between two stored energies, not the energy at some average voltage.

Equation. $E = \frac{1}{2}CV^2$, so $\Delta E = \frac{1}{2}C(V_2^2 - V_1^2)$.

Substitute. $\Delta E = \frac{1}{2} \times 45 \times 10^{-6} \times (9.6^2 - 8.0^2)$.

Answer. $\Delta E = 6.3 \times 10^{-4} \text{ J}$.

Solution 4

Check. Square each voltage **before** subtracting. Squaring the difference, $(9.6 - 8.0)^2 = 2.56$, gives 5.8×10^{-5} J: about a tenth of the true value, and wrong for the same reason $(a - b)^2 \neq a^2 - b^2$.

Mark scheme

- $E = \frac{1}{2} CV^2$
- $\Delta E = \frac{1}{2} \times 45 \times 10^{-6} (9.6^2 - 8.0^2)$
- $= 6.3 \times 10^{-4}$ J

Solution 4

(c)(i)

Mark scheme

- gaps in circuit closed and correct symbol for capacitor shown in parallel with load resistor

Solution 4

(c)(ii) Worked steps

Know. Between the peaks of the rectified supply the capacitor discharges through the load, so the falling part of each ripple is an exponential decay with time constant τ .

Read two points. Take both from **within one** falling section, for example (5.0 ms, 4.0 V) and (13.0 ms, 3.2 V), so $\Delta t = 8.0$ ms.

Equation. $V = V_0 \exp\left(-\frac{\Delta t}{\tau}\right)$.

Solution 4

Substitute. $3.2 = 4.0 \exp\left(-\frac{8.0}{\tau}\right)$, so $\ln\left(\frac{3.2}{4.0}\right) = -\frac{8.0}{\tau}$.

Answer. $\tau = 36$ ms.

Solution 4

Check. Both read-offs must come from the **same** discharge, between one peak and the next. Taking V_0 from one ripple and V from a later one measures a decay that the recharging has already interrupted, and the time constant comes out far too large.

Mark scheme

- two correct pairs of values of t and V read off from within same discharge cycle, e.g. (5.0, 4.0) and (13.0, 3.2)
- correct substitution of values of V , V_0 and Δt into $V = V_0 \exp(-\Delta t/\tau)$
- e.g. $3.2 = 4.0 \exp(-8.0/\tau)$
- $\tau = 36 \text{ ms}$

Solution 4

(d)(i)

Mark scheme

- 8.0 W

(d)(ii)

Mark scheme

- 4.0 W

Question 5

9702/42 M23 ■ Q5 ■ 10 marks

A capacitor, a battery of electromotive force (e.m.f.) 12 V, a resistor R and a two-way switch are connected in the circuit shown in Fig. 5.1.

The switch is initially in position S. When the capacitor is fully charged, the switch is moved to position T so that the capacitor discharges. At time t after the switch is moved the charge on the capacitor is Q .

The variation with t of $\ln(Q/\mu\text{C})$ is shown in Fig. 5.2.


- (a) Show that the capacitance of the capacitor is $1.5\ \mu\text{F}$. [3]
- (b) Determine the resistance of R . [3]
- (c) Calculate the energy stored in the capacitor at time $t = 0$. [2]
- (d) A second identical resistor is now connected in parallel with R .

Question 5

The switch is initially in position S. When the capacitor is fully charged, the switch is moved to position T so that the capacitor discharges. At time t after the switch is moved the charge on the capacitor is Q .

On Fig. 5.2, sketch a line to show the variation of $\ln(Q/\mu\text{C})$ with t between time $t = 0$ and time $t = 5.0 \text{ s}$. **[2]**

Question 5

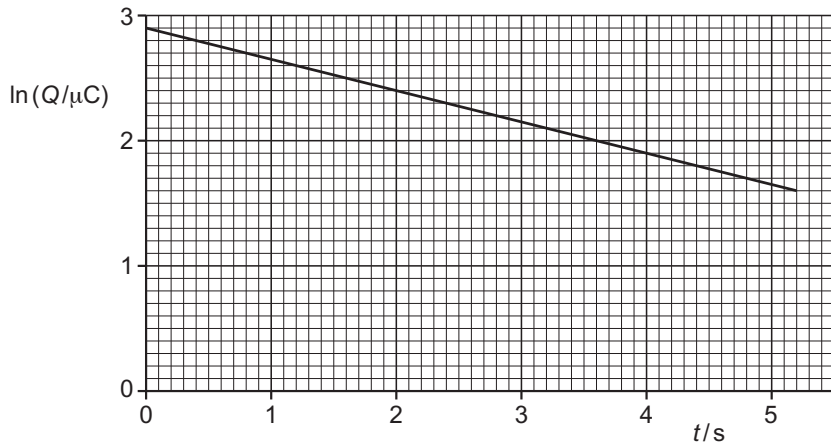

Solution 5

(a) Worked steps

Know. The graph is of $\ln Q$ against t , so the **intercept** gives the charge at $t = 0$, which is the fully charged value.

Read the intercept. $\ln\left(\frac{Q}{\mu\text{C}}\right) = 2.9$ at $t = 0$, so $Q = e^{2.9} = 18 \mu\text{C}$.

Equation. $C = \frac{Q}{V}$, with V the e.m.f. the capacitor was charged to, 12 V.

Substitute. $C = \frac{18.2 \times 10^{-6}}{12}$.

Solution 5

Answer. $C = 1.5 \times 10^{-6} \text{ F} = 1.5 \text{ } \mu\text{F}$, as required.

Check. The vertical axis is a **logarithm**, so 2.9 is not a charge. Reading it as $2.9 \text{ } \mu\text{C}$ gives $0.24 \text{ } \mu\text{F}$ and loses all three marks.

Mark scheme

- from graph $\ln Q = 2.9$
- (so $Q = 18.2 \text{ } \mu\text{C}$)
- $C = Q/V$
- $= 18.2/12 = 1.5 \text{ } \mu\text{F}$

Solution 5

(b) Worked steps

Know. Taking logs of $Q = Q_0 \exp\left(-\frac{t}{RC}\right)$ gives $\ln Q = \ln Q_0 - \frac{t}{RC}$. That is the equation of a straight line whose gradient is $-\frac{1}{RC}$, which is why the graph was drawn this way.

Measure the gradient. From the line, gradient $= -0.25 \text{ s}^{-1}$.

Equation. gradient $= -\frac{1}{RC}$, so $R = \frac{1}{0.25 C}$.

Substitute. $R = \frac{1}{0.25 \times 1.5 \times 10^{-6}}$.

Answer. $R = 2.7 \times 10^6 \Omega$.

Solution 5

Check. Use the capacitance in **farads**, not microfarads. And take the gradient from the drawn line over a large triangle, not from two crowded points: the whole reason for plotting logs is that a straight line can be measured accurately. [Mark scheme](#)

- gradient = -0.25
- gradient = $-1/RC$
- $R = 1/(0.25 \times 1.5 \times 10^{-6})$
- $= 2.7 \times 10^6 \Omega$
- **or**
- $\frac{Q}{Q_0} = e^{-t/CR}$ or $\ln Q - \ln Q_0 = -\frac{t}{CR}$

Solution 5

- e.g. $\frac{4.95}{18.2} = e^{-5.2/(1.5 \times 10^{-6} R)}$ or $1.6 - 2.9 = 5.2/(1.5 \times 10^{-6} R)$
- $R = 2.7 \times 10^6 \Omega$

Solution 5

(c) Worked steps

Know. At $t = 0$ the capacitor is fully charged, so use the values already found:
 $Q = 18 \mu\text{C}$ at $V = 12 \text{ V}$.

Equation. $W = \frac{1}{2}QV$ (or equally $\frac{1}{2}CV^2$, or $\frac{Q^2}{2C}$ — all three give the same number).

Substitute. $W = \frac{1}{2} \times 18.2 \times 10^{-6} \times 12$.

Answer. $W = 1.1 \times 10^{-4} \text{ J}$.

Check. The factor of $\frac{1}{2}$ is not optional. QV alone would be the work done by the battery; half of that ends up in the capacitor and the other half is dissipated in the circuit resistance while charging. [Mark scheme](#)

Solution 5

- $W = \frac{1}{2}QV$
- $= \frac{1}{2} \times 18.2 \times 10^{-6} \times 12$
- $= 1.1 \times 10^{-4} \text{ J}$
- or $W = \frac{1}{2}CV^2$
- $= \frac{1}{2} \times 1.5 \times 10^{-6} \times 12^2$
- $= 1.1 \times 10^{-4} \text{ J}$
- or $W = \frac{1}{2}Q^2/C$
- $= \frac{1}{2} \times (18.2 \times 10^{-6})^2 / 1.5 \times 10^{-6}$
- $= 1.1 \times 10^{-4} \text{ J}$

Solution 5

(d) Worked steps

Know. Two identical resistors in parallel have **half** the resistance of one, so the time constant RC is halved and the capacitor discharges **twice as fast**.

Start point. The initial charge is unchanged: the capacitor is charged by the same 12 V battery through the same switch. So the new line starts at the same intercept, (0, 2.9).

Gradient. The gradient is $-\frac{1}{RC}$, and R has halved, so the new gradient is **twice as steep** and still negative: about -0.50 s^{-1} .

Draw. A straight line from (0, 2.9) falling twice as steeply as the original, drawn at least as far as $t = 5.0 \text{ s}$.

Solution 5

Check. Two straight lines from the same intercept, one steeper than the other, is the whole answer. A curve would mean the discharge is no longer exponential, and putting the resistors in parallel does not change that.

Mark scheme

- straight line with different negative gradient starting from $(0, 2.9)$
- straight line between $t = 0$ and at least $t = 5.0\text{s}$ with twice the gradient of the original line