

10.1 Practical circuits

Name: _____ Class: _____ Date: _____

Total: 14 marks

KEY WORDS resistance 电阻 • internal resistance 内阻 • terminal p.d. 端电压 • open circuit 开路
• cell 电池

Objective

Build the skills to answer exam questions on **practical circuits** — e.m.f., p.d., and internal resistance.

You must be able to:

- define **e.m.f.** and distinguish it from **p.d.**
- explain **internal resistance** and use $V = \varepsilon - Ir$
- describe how to measure internal resistance

1 Worked examples


Study these first. Each one shows the method for a question type used later — follow the steps and you can do the Practice and Exam-style questions yourself.


■ e.m.f. and p.d.

e.m.f. ε = energy given to each coulomb by the source (in driving it round the whole circuit). **p.d.** = energy transferred from electrical form by each coulomb in a component. Both in volts.

■ Internal resistance

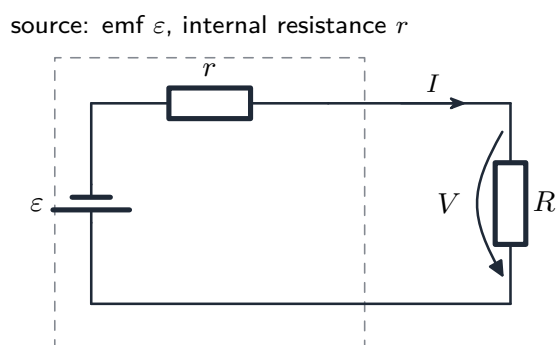A real cell has **internal resistance** r . When current flows, Ir is "lost" inside it, so the **terminal p.d.** is:



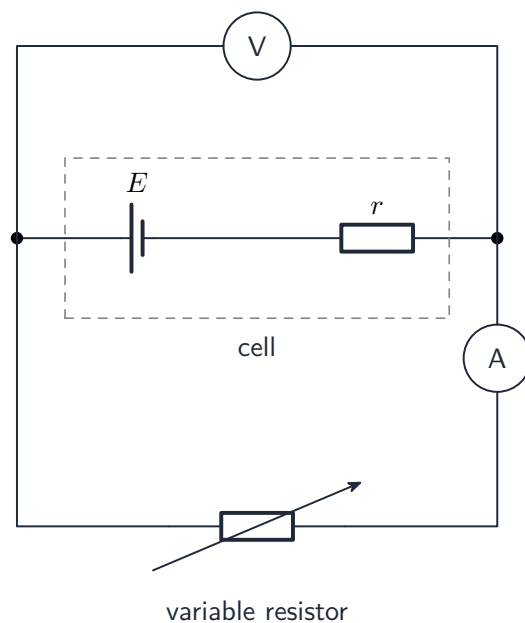

Internal resistance in a practical cell

$$V = \varepsilon - Ir.$$

- $I = 0$ (open circuit): $V = \varepsilon$;
- larger current $\rightarrow$ smaller terminal p.d.

Worked example. $\varepsilon = 1.5 \text{ V}$, $r = 0.50 \text{ } \Omega$, $R = 2.5 \text{ } \Omega$: $I = \frac{\varepsilon}{R + r} = \frac{1.5}{3.0} = 0.50 \text{ A}$;
 $V = \varepsilon - Ir = 1.5 - 0.25 = 1.25 \text{ V}$.

To **measure** r : vary R , plot V against I — the intercept is ε and the gradient is $-r$.

2 Practice

Now apply the methods above.

2.1 Define the **e.m.f.** of a source. [1]

2.2 Write the equation linking **terminal p.d.**, e.m.f., current and internal resistance. [1]

2.3 State the terminal p.d. of a cell when **no current** flows. [1]

2.4 State **one** cause of a cell's internal resistance. [1]

3 Exam-style questions

3.1 A battery of e.m.f. 9.0 V drives two resistors, of $12\ \Omega$ and $6.0\ \Omega$, connected in **parallel** with each other. The terminal p.d. is measured as 8.0 V . **Determine** the internal resistance of the battery, and the energy wasted inside it each second. [5]

3.2 As the current drawn from a cell **increases**, the terminal p.d.: [1]

- **A** increases
- **B** decreases
- **C** stays the same
- **D** becomes equal to the e.m.f.

3.3 Explain, in terms of **energy**, the difference between e.m.f. and p.d. [2]

3.4 Describe how a graph can be used to find the **internal resistance** of a cell. [2]

Solutions

2.1 The **energy transferred per unit charge** by the source in driving charge **around the complete circuit**.

2.2 $V = \varepsilon - Ir$.

2.3 Equal to the **e.m.f.** ε .

2.4 Any one: the resistance of the **electrolyte** in a cell; the resistance of the **wire windings** in a generator.

3.1 External resistance: $\frac{1}{R} = \frac{1}{12} + \frac{1}{6.0}$, so $R = 4.0 \, \Omega$. The terminal p.d. is across that combination, so $I = \frac{8.0}{4.0} = 2.0 \, \text{A}$. The "lost volts" are $9.0 - 8.0 = 1.0 \, \text{V}$, so $r = \frac{1.0}{2.0} = 0.50 \, \Omega$. Energy wasted per second $= I^2 r = (2.0)^2(0.50) = 2.0 \, \text{W}$, i.e. $2.0 \, \text{J}$ each second.

3.2 **B** — decreases (more Ir is lost internally).

3.3 **e.m.f.** is energy put **into** the circuit per coulomb by the source; **p.d.** is energy taken **out** of the electrical form per coulomb in a component.

3.4 Vary the external resistance and measure V and I ; plot V against I — the magnitude of the **gradient** is r (and the intercept is ε).