

# 10.3 Potential dividers

Name: \_\_\_\_\_ Class: \_\_\_\_\_ Date: \_\_\_\_\_

**Total: 19 marks**

**KEY WORDS** null method 零点法 • potential divider 分压器 • galvanometer 检流计 • potentiometer 电位差计  
• thermistor 热敏电阻

## Objective

Build the skills to answer exam questions on **potential dividers** — the divider equation, the uniform wire, and sensor circuits.

**You must be able to:**


- use the **potential divider** equation
- explain why p.d. is proportional to **length** on a **uniform** wire ( $V \propto L$ )
- explain **thermistor** and **LDR** divider circuits, and the potentiometer null method


## 1 Worked examples

Study these first. Each one shows the method for a question type used later — follow the steps and you can do the Practice and Exam-style questions yourself.
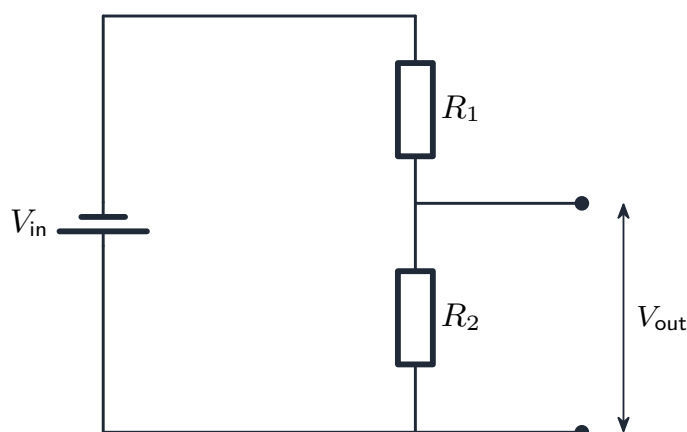
### ■ Potential divider

Two resistors in series share  $V_{\text{in}}$  in proportion to their resistances. The output across  $R_2$  is:



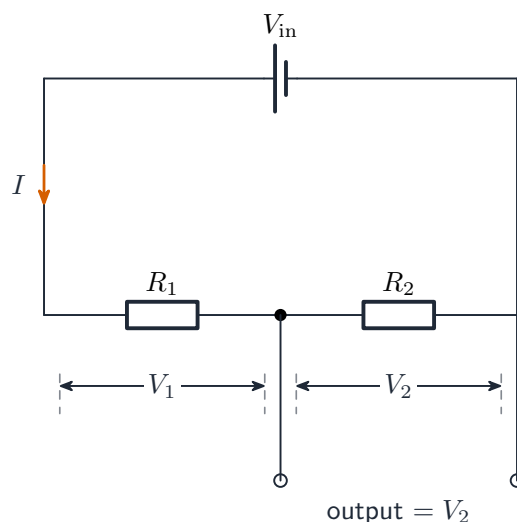

*A potential divider splits the voltage*

$$V_{\text{out}} = V_{\text{in}} \cdot \frac{R_2}{R_1 + R_2}.$$

**Worked example.** 6.0 V across 2.0 k $\Omega$  + 4.0 k $\Omega$ , output across the 4.0 k $\Omega$ :  $V_{\text{out}} = 6.0 \times \frac{4.0}{6.0} = 4.0$  V.

#### ■ Uniform wire: $V \propto L$

A **uniform** resistance wire has the same resistance per unit length, so resistance is proportional to length ( $R = \rho L/A$  with  $\rho, A$  constant). A length of wire is just a potential divider, so the **p.d. across a length is proportional to that length**:

$$V = V_{\text{wire}} \cdot \frac{L}{L_{\text{total}}}.$$

**Worked example.** A 2.0 V supply is across a uniform wire of length 100 cm. The p.d. across the first 30 cm is  $V = 2.0 \times \frac{30}{100} = 0.60$  V. This  $V \propto L$  rule is the basis of the **potentiometer**.

#### ■ Sensor circuits

Replace a resistor with a **sensor**: a **thermistor** ( $R$  falls as temperature rises) or an **LDR** ( $R$  falls as light rises). The output voltage then changes with temperature or light, and can switch a load.

#### ■ Potentiometer

A uniform wire with a sliding contact compares e.m.f.s by a **null method**: slide until a **galvanometer** reads **zero** (no current), so the balance lengths are in the ratio of the e.m.f.s.

## 2 Practice

---

Now apply the methods above.

**2.1** State what a **potential divider** does. [1]

---

**2.2** A 6.0 V supply is across a 2.0 k $\Omega$  and a 4.0 k $\Omega$  resistor in series. Find the p.d. across the 4.0 k $\Omega$  resistor. [2]

**2.3** A uniform wire of length 80 cm has 4.0 V across its ends. Find the p.d. across the first 20 cm. [2]

**2.4** State what happens to a **thermistor's** resistance as temperature rises. [1]

---

## 3 Exam-style questions

---

**3.1** A 12 V supply is across  $R_1 = 3.0$  k $\Omega$  and  $R_2 = 1.0$  k $\Omega$  in series. Find  $V_{\text{out}}$  taken across  $R_2$ . [2]

**3.2** A 6.0 V supply of negligible internal resistance is connected to a variable resistor  $R$  in series with a uniform resistance wire XY of resistance 8.0  $\Omega$ .

(a)  $R$  is adjusted so the p.d. across XY is 2.4 V. Calculate  $R$ . [3]

(b) Explain why the p.d. between any two points on wire XY is **proportional to the distance** between them. [2]

---

---

**3.3** In a divider, a thermistor is in series with a fixed resistor and the output is taken across the **thermistor**. The temperature **rises**. Explain what happens to the output voltage. [3]

---

---

---

**3.4** Explain how an **LDR** in a potential divider can be used to switch a lamp **on** when it gets dark. [3]

---

---

---

## Solutions

---

**2.1** Splits an input voltage into a chosen smaller output voltage, sharing it between resistors in proportion to their resistances.

**2.2**  $V = 6.0 \times \frac{4.0}{2.0 + 4.0} = 4.0 \text{ V}.$

**2.3**  $V = 4.0 \times \frac{20}{80} = 1.0 \text{ V}.$

**2.4** It **decreases**.

**3.1**  $V_{\text{out}} = 12 \times \frac{1.0}{3.0 + 1.0} = 12 \times 0.25 = 3.0 \text{ V}.$

**3.2** (a) The wire and  $R$  form a potential divider:  $V_{XY} = \varepsilon \cdot \frac{R_{XY}}{R + R_{XY}}$ , so  $2.4 = 6.0 \times \frac{8.0}{R + 8.0}$ ;  $R + 8.0 = \frac{6.0 \times 8.0}{2.4} = 20$ ;  $R = 12 \text{ } \Omega$ .

**3.2** (b) The wire is **uniform**, so its resistance is **proportional to length**; the same current flows along it, so by  $V = IR$  the p.d. across a length is proportional to that length.

**3.3** As temperature rises, the thermistor's resistance **decreases**; it now takes a **smaller share** of the total voltage; so the output voltage across the thermistor **decreases**.

**3.4** Put the **LDR** in series with a fixed resistor and take the output across the **fixed resistor** (so the output rises in the dark); as it gets dark the LDR's resistance **rises**, so a larger share of the voltage is across the fixed resistor and the output **rises**; the output crosses a **threshold** that switches the lamp on (e.g. via a transistor/comparator).