

# 19.3 Discharging a capacitor

Name: \_\_\_\_\_ Class: \_\_\_\_\_ Date: \_\_\_\_\_

Total: 29 marks

**KEY WORDS** time constant 时间常数 • exponential decay 指数衰减 • resistor 电阻器 • resistance 电阻  
• capacitor 电容器

## Objective

Build the skills to answer exam questions on a **capacitor discharging** through a resistor.

**You must be able to:**


- use the **time constant**  $\tau = RC$
- use  $x = x_0 e^{-t/RC}$  for charge, p.d. or current
- interpret the discharge graphs


## 1 Worked examples

Study these first. Each one shows the method for a question type used later — follow the steps and you can do the Practice and Exam-style questions yourself.
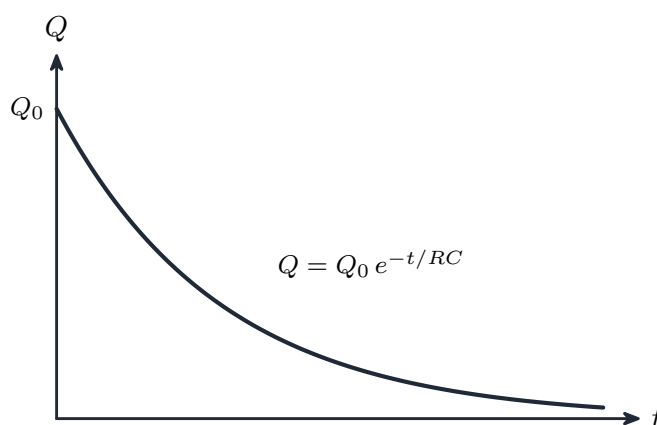
### ■ Exponential decay

When a charged capacitor discharges through a resistor, the charge (and  $V$ ,  $I$ ) decays **exponentially**:



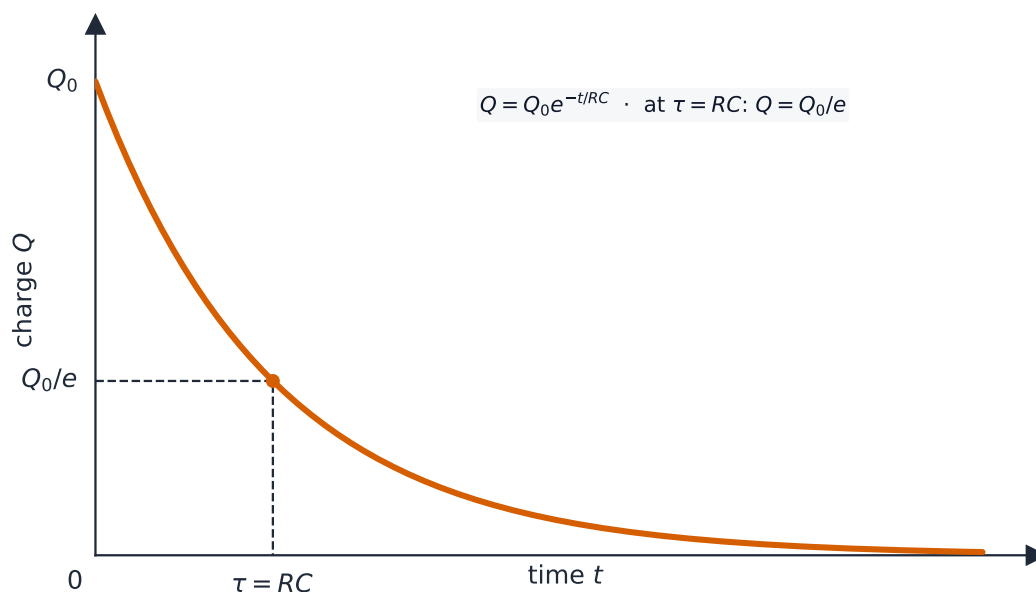

*Exponential discharge of a capacitor*

$$Q = Q_0 e^{-t/RC}, \quad V = V_0 e^{-t/RC}, \quad I = I_0 e^{-t/RC}.$$

The **time constant**  $\tau = RC$  is the time for the charge to fall to  $\frac{1}{e} \approx 37\%$  of its initial value.

**Worked example.**  $470 \mu\text{F}$  through  $2.0 \text{ k}\Omega$ :  $\tau = RC = (2000)(470 \times 10^{-6}) = 0.94 \text{ s}$ .

#### ■ Finding the time — take logs

To find the **time** for the charge (or  $V$ , or  $I$ ) to fall to a given value, take the **natural log** of both sides of  $V = V_0 e^{-t/RC}$ :

$$\ln \frac{V}{V_0} = -\frac{t}{RC} \quad \Rightarrow \quad t = -RC \ln \frac{V}{V_0}.$$

**Worked example.** For the capacitor above (charged to  $6.0 \text{ V}$ ,  $\tau = 0.94 \text{ s}$ ), the time for the p.d. to fall to  $2.0 \text{ V}$  is  $t = -0.94 \ln \frac{2.0}{6.0} = -0.94 \times (-1.10) = 1.0 \text{ s}$ .

## 2 Practice

---

Now apply the methods above.

**2.1** Write the formula for the **time constant**. [1]

---

**2.2** A  $100\ \mu\text{F}$  capacitor discharges through a  $10\ \text{k}\Omega$  resistor. Find the **time constant**. [2]

**2.3** State what happens to the **charge** as a capacitor discharges. [1]

---

**2.4** Write the discharge equation for **charge**. [1]

---

## 3 Exam-style questions


---

**3.1** The time constant  $RC$  is the time for the charge to fall to: [1]

- **A** zero
  - **B** half its initial value
  - **C**  $1/e$  (about 37%) of its initial value
  - **D**  $1/2e$  of its initial value
- 


**3.2** A  $470\ \mu\text{F}$  capacitor charged to  $6.0\ \text{V}$  discharges through a  $2.0\ \text{k}\Omega$  resistor. Calculate (a) the time constant, (b) the p.d. after  $1.0\ \text{s}$ . [4]

 **3.3** Sketch a graph of **charge against time** for a discharging capacitor. [2]



**3.4** State what happens to the time constant if the **resistance** is doubled. [1]

 **3.5** A  $220\ \mu\text{F}$  capacitor charged to  $9.0\ \text{V}$  discharges through a  $15\ \text{k}\Omega$  resistor. Calculate the **time** for the p.d. to fall to  $3.0\ \text{V}$ . [4]




**3.6** A capacitor  $C$  is charged and then discharged through a resistor  $R$ . A data logger records the p.d.  $V_R$  across the resistor and the p.d.  $V_C$  across the capacitor. At  $t = 0$  the p.d. across the capacitor is  $9.0\ \text{V}$ , and the initial current is  $1.8\ \text{mA}$ . The p.d. across the capacitor falls to  $3.3\ \text{V}$  after  $12\ \text{s}$ .

(a) **State** the relationship between  $V_C$  and  $V_R$  during the discharge, and give a reason. [2]



 (b) **Determine** the resistance  $R$ . [2]



(c) **Determine** the time constant  $\tau$  of the circuit. [3]

(d) Hence **determine** the capacitance  $C$ , in  $\mu\text{F}$ . [2]

(e) **Explain**, in terms of the current in the circuit, why the decay of the charge on the capacitor is **exponential**. [3]

## Solutions

---

**2.1**  $\tau = RC$ .

**2.2**  $\tau = RC = (10 \times 10^3)(100 \times 10^{-6}) = 1.0 \text{ s}$ .

**2.3** It **decreases exponentially** towards zero.

**2.4**  $Q = Q_0 e^{-t/RC}$ .

**3.1**  $C = 1/e$  (about 37%).

**3.2** (a)  $\tau = RC = (2.0 \times 10^3)(470 \times 10^{-6}) = 0.94 \text{ s}$ . (b)  $V = V_0 e^{-t/RC} = 6.0 e^{-1.0/0.94} = 6.0 \times 0.345 = 2.1 \text{ V}$ .

**3.3** A curve starting at the initial charge and **decaying exponentially** towards zero, with the same shape (never quite reaching zero).

**3.4** It **doubles** ( $\tau = RC$ ).

**3.5**  $\tau = RC = (15 \times 10^3)(220 \times 10^{-6}) = 3.3 \text{ s}$ ;  $t = -RC \ln \frac{V}{V_0} = -3.3 \ln \frac{3.0}{9.0} = -3.3 \times (-1.10) = 3.6 \text{ s}$ .

**3.6** (a) They are **equal** at every instant,  $V_C = V_R$ , because the capacitor and resistor form a single loop with no other source, so the p.d. driving the current is the capacitor's own p.d..

(b)  $R = \frac{V}{I} = \frac{9.0}{1.8 \times 10^{-3}} = 5.0 \times 10^3 \Omega$ .

(c)  $V = V_0 e^{-t/\tau}$ , so  $\frac{3.3}{9.0} = e^{-12/\tau}$ ;  $\ln(0.367) = -\frac{12}{\tau}$ , giving  $-1.003 = -\frac{12}{\tau}$  and  $\tau = 12 \text{ s}$ . (The p.d. has fallen to  $1/e$  of its start, which is what the time constant means.)

(d)  $\tau = RC$ , so  $C = \frac{12}{5.0 \times 10^3} = 2.4 \times 10^{-3} \text{ F} = 2.4 \times 10^3 \mu\text{F}$ .

(e) The current is  $I = \frac{V_C}{R}$ , and  $V_C \propto Q$ , so the current — the rate at which charge leaves — is **proportional to the charge still on the capacitor**. A quantity whose rate of decrease is proportional to itself decays exponentially; so as the charge falls the current falls with it, the discharge slows, and  $Q$  never quite reaches zero.