

Question 31 (Answer: **D**)

- Power is $P = VI$, and Ohm's law gives $I = V/R$.
- Substituting: $P = V \times V/R = V^2/R$.
- $P = I^2 R$ is the other valid form; A and B mix the two together.

Question 32 (Answer: **D**)

- With the resistance constant, $P = I^2 R$, so the power goes as the *square* of the current.
- $(12.0/8.0)^2 = 1.5^2 = 2.25$.
- The new power is $2.3P$; C assumes it scales with I rather than I^2 .

Question 34 (Answer: **D**)

- Read the branches: PQ is two resistors in series ($2R$) and RS is two in parallel ($R/2$).
- So the top path P-Q-R is $3R$ and the bottom path P-S-R is $1.5R$ – the bottom path carries twice the current.
- $P = I^2 R$, so SP (a full resistor at the larger current) dissipates $4V^2/9R$, beating PQ and RS at $2V^2/9R$.

Question 30 (Answer: **B**)

- Potential difference is the energy transferred per unit charge.
- So $1 \text{ V} = 1 \text{ J C}^{-1}$.
- A is the ampere, C is the watt, and D (J s C^{-2}) is the ohm.

6(a)	energy transferred (to the component) per (unit) charge
6(b)(i)	$Q = It$ $= 0.030 \times 4.0 \times 60$
	$= 7.2 \text{ C}$
6(b)(ii)	$I = V/R$ $I_1 = 8.0/(430+240)$
	$= 0.012 \text{ A}$
6(b)(iii)	$I_2 = 0.030 - I_1$ $= 0.030 - 0.012$ $= 0.018 \text{ A}$

6(b)(iv)	$R = V/I_2$ $= (8.0 - (0.018 \times 210))/0.018$
	$= 230 \Omega$
	OR resistance of top branch $= 8.0/0.018$ $R = 8.0/0.018 - 210$
	$= 230 \Omega$
	OR total circuit resistance $= 8.0/0.030 = 267$ $1/267 = 1/(210 + R) + 1/(430 + 240)$ $1/267 - 1/670 = 1/(210 + R)$ $210 + R = 443$
	$R = 230 \Omega$
6(c)	(When) the galvanometer reads 0 (A)
	The ratio of the resistances in the top branch will equal the ratio of the resistances in the bottom branch (so the resistance of X can be determined)
	OR The ratio of the left pair of resistances will equal the ratio of the right pair of resistances