

A-Level Physics

Name: _____ Score: _____

1. Capacitance is the charge stored per unit:

- ☐ potential difference
- ☐ current
- ☐ resistance
- ☐ time

2. The energy stored in a capacitor is:

- ☐ $\frac{1}{2}CV^2$
- ☐ CV^2
- ☐ $\frac{1}{2}CV$
- ☐ $\frac{1}{2}QV^2$

3. During discharge through a resistor, the charge on a capacitor:

- ☐ decays exponentially
- ☐ falls in a straight line
- ☐ stays constant
- ☐ rises steadily

4. A capacitor holds 0.012 C at 4.0 V. What is its capacitance, in mF?

_____ mF

5. A 2.0 μF capacitor is charged to 1000 V. How much energy does it store?

_____ J

6. The charge during discharge is given by:

- ☐ $Q_0e^{-t/RC}$
- ☐ $Q_0e^{t/RC}$
- ☐ $Q_0(1 - e^{-t/RC})$
- ☐ $\frac{Q_0}{t}$

7. Doubling the charge on a capacitor doubles the voltage, so its capacitance stays the same.

- ☐ True ☐ False

8. Why is there a factor of $\frac{1}{2}$ in the stored-energy formula?

- ☐ the average p.d. during charging is only $V/2$
- ☐ half the charge leaks away
- ☐ the capacitor is only half full
- ☐ energy is always halved

9. A capacitor of $500\ \mu\text{F}$ discharges through a $2000\ \Omega$ resistor. What is the time constant?

_____ s

10. A $2.0\ \mu\text{F}$ and a $3.0\ \mu\text{F}$ capacitor are in parallel. What is the total capacitance, in μF ?

_____ μF

A-Level Physics

1. potential difference

$C = \frac{Q}{V}$ — charge per volt, in farads.

2. $\frac{1}{2}CV^2$

Equivalent forms: $W = \frac{1}{2}QV = \frac{1}{2}CV^2 = \frac{Q^2}{2C}$.

3. decays exponentially

The bigger the charge, the bigger the current — giving an exponential decay.

4. 3 mF

$C = \frac{Q}{V} = \frac{0.012}{4.0} = 0.0030 \text{ F} = 3.0 \text{ mF}$.

5. 1 J

$W = \frac{1}{2}CV^2 = \frac{1}{2} \times 2.0 \times 10^{-6} \times (1000)^2 = 1.0 \text{ J}$.

6. $Q_0e^{-t/RC}$

Discharge falls toward zero: $Q = Q_0e^{-t/RC}$ (the $1 - e^{-t/RC}$ form is for *charging*).

7. True

$C = \frac{Q}{V}$ is fixed by the capacitor's size and dielectric — Q and V rise together.

8. the average p.d. during charging is only $V/2$

The p.d. rises from 0 to V as it charges, so the average is $V/2$ — hence the triangle area $\frac{1}{2}QV$.

9. 1 s

$\tau = RC = 2000 \times 500 \times 10^{-6} = 1.0 \text{ s}$.

10. 5 μF

In parallel capacitances add: $2.0 + 3.0 = 5.0 \mu\text{F}$.