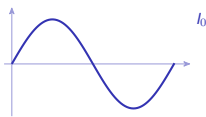


Alternating Currents

A2 Physics ■ Topic 21

A-Level Physics



Alternating Currents

What we will cover

- 1 Alternating current basics
- 2 Power in a resistor
- 3 Root-mean-square values
- 4 Rectification and smoothing
- 5 Recap

1 AC basics



Alternating Currents


AC basics

Current that keeps reversing

An **alternating current** 交流电 keeps reversing direction. Mains is sinusoidal:

$$I = I_0 \sin(\omega t), \quad V = V_0 \sin(\omega t)$$

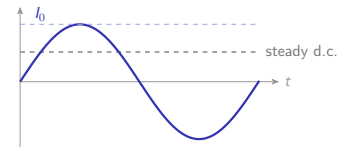
For a purely resistive load, V and I are in phase.



Alternating Currents

AC basics

Alternating current basics

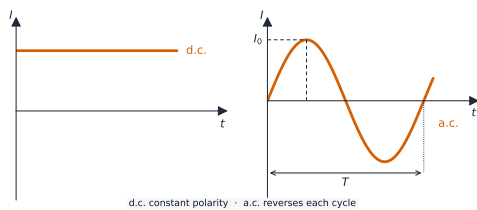


A steady direct current compared with a sinusoidal alternating current of peak I_0 and period T


Alternating Currents

AC basics

The words on a CRO trace

- period T** time for one full cycle. $f = 1/T$. Mains is 50 or 60 Hz.
- angular frequency** $\omega = 2\pi f = 2\pi/T$
- peak I_0 or V_0** the largest value in a cycle (amplitude)
- peak-to-peak** $2I_0$ – from $+I_0$ to $-I_0$; useful on a CRO

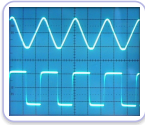Alternating Currents AC basics The values you read off an a.c. trace Peak value The peak value 峰值 I_0 or V_0: the largest value in a cycle – the amplitude. Peak-to-peak value The peak-to-peak value 峰峰值 $2I_0$: from $+I_0$ down to $-I_0$, which is what a CRO screen shows most directly. Period and frequency One cycle spans the period T; the frequency is $f = 1/T$. Read T off the time-base setting. R.m.s. value $V_{rms} = V_0/\sqrt{2}$: the d.c. voltage that would deliver the same mean power in the same resistance 电阻. Mains "230 V" is an r.m.s. value; the peak is about 325 V, and insulation has to survive the peak.	Alternating Currents AC basics Reading a CRO Same as any wave (Topic 7), using a cathode-ray oscilloscope 示波器: - horizontal divisions $\times$ time-base 时基 $\rightarrow$ period T, so $f = 1/T$ - vertical divisions $\times$ y-gain $\rightarrow$ peak voltage V_0 (centre to peak, or peak-to-peak then halve) 
---	---

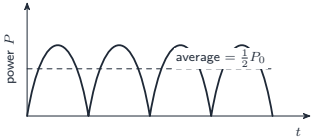2 Power	Alternating Currents Power Power in a resistor pulses at $2f$ Instant power $P(t) = I(t)^2 R$. With $I = I_0 \sin(\omega t)$: $P(t) = I_0^2 R \sin^2(\omega t)$ Always positive; peak $I_0^2 R$; minimum zero; oscillates at twice the frequency of I. The mean of $\sin^2$ over a cycle is $\frac{1}{2}$, so $\langle P \rangle = \frac{1}{2} I_0^2 R = \frac{1}{2} P_{\text{peak}}$  Average a.c. power in a resistor is half the peak power.
--	--


Alternating Currents Power Why r.m.s. matters "230 V mains" means $V_{r.m.s.} = 230$ V, with peak $V_0 = 230\sqrt{2} \approx 325$ V. Components must be rated for the peak, not the r.m.s.	Alternating Currents Power Drawing the diagrams - half-wave: a.c. source – single diode – load R, in series. - full-wave bridge: four diodes as the arms of a "diamond"; the a.c. input goes to one pair of opposite corners, the load R across the other pair.
--	--

3 Root-mean-square

Alternating Currents
└ Root-mean-square

r.m.s. is the equivalent steady d.c.

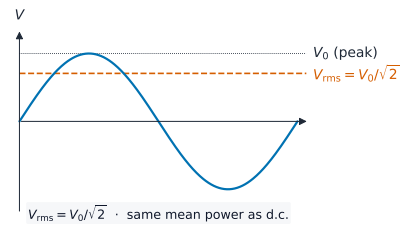$I_{r.m.s.}$ is the steady direct current giving the same average power in the same R : $I_{r.m.s.} = I_0/\sqrt{2}$, $V_{r.m.s.} = V_0/\sqrt{2}$.




4 Rectification

Alternating Currents
└ Rectification

The rectified output

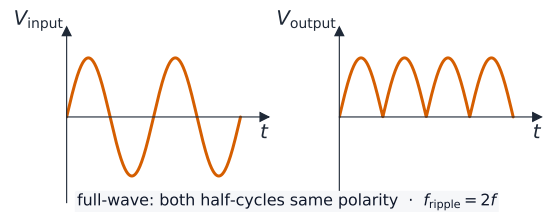
Full-wave flips the negative half rather than discarding it, so the output never rests at zero and its mean is **twice** the half-wave value.



Alternating Currents
└ Rectification

Smoothing – a capacitor across the load

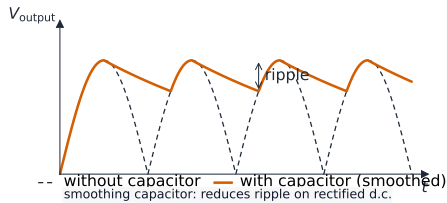The capacitor charges to near the peak, then **discharges through the load** (time constant RC) while the diodes are cut off. The dips left are the **ripple** 纹波: smaller for larger C , larger R , or full-wave rectification.



Alternating Currents
└ Rectification

How it works


- on the **rising part** of each pulse, the capacitor charges up to near the peak.
- on the **falling part** (and any gap), the diodes are reverse-biased, so the capacitor **discharges through the load**, keeping current flowing.
- at the next peak, the capacitor charges again, and the cycle repeats.

Purpose in summary

The smoothing capacitor reduces the ripple, giving a steadier d.c.


voltage suitable for sensitive electronics.

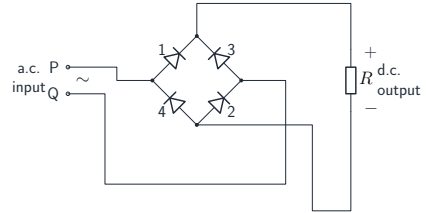Full-wave rectification (bridge rectifier)



A four-diode bridge sends the load current the same way whichever a.c. terminal is positive

Half-wave rectification

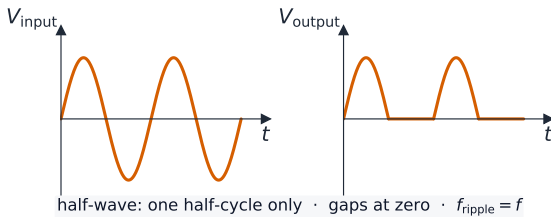

In half-wave rectification a single diode passes only the positive half-cycles

Worked example – r.m.s. values in use

(a) An a.c. supply has a peak voltage of 12 V: find its r.m.s. voltage. (b) A $50\ \Omega$ heater runs on the 230 V r.m.s. mains: find the r.m.s. current and the average power.

- (a) $V_{\text{rms}} = V_0 / \sqrt{2} = 12 / \sqrt{2} \approx 8.5\ \text{V}$.
- (b) $I_{\text{rms}} = V_{\text{rms}} / R = 230 / 50 = 4.6\ \text{A}$.
- $\langle P \rangle = V_{\text{rms}} I_{\text{rms}} = 230 \times 4.6 \approx 1.06\ \text{kW}$.

Use r.m.s. values for power, peak values for insulation. Mixing them is the standard error here.

Exam tips

- $I_{\text{rms}} = I_0 / \sqrt{2}$ for a sinusoidal current; use r.m.s. values for power ($P = I_{\text{rms}}^2 R$).
- Mean power in a resistor = $\frac{1}{2}$ of the peak power.
- Explain **rectification** (diode or bridge) and how a **smoothing capacitor** reduces the ripple.

5 Recap

Topic 21 – key takeaways

1 a.c.

$$I = I_0 \sin(\omega t); f = 1/T; \omega = 2\pi f$$

2 r.m.s.

$$I_{\text{rms}} = I_0 / \sqrt{2}; \text{ power uses r.m.s.}$$

3 Rectify

one diode (half) or four-diode bridge (full)

4 Smooth

C in parallel with R ; large $RC \Rightarrow$ small ripple

Check yourself

- 1 Peak of 230 V r.m.s. mains?
- 2 Average power in a resistor, as a fraction of peak power?
- 3 How many diodes in a bridge rectifier?
- 4 Two ways to reduce ripple?

Answers 1. $\approx 325 \text{ V}$ 2. half 3. four 4. larger C or R , or full-wave (higher frequency)