

## Exercise walk-through

### Kirchhoff's Loop Rule ■ 11.6

eXercise

## You must be able to

- state **Kirchhoff's loop rule** 基尔霍夫电压定律: the sum of potential differences around any closed loop is zero
- explain the loop rule as a statement of **conservation of energy** 能量守恒
- apply the loop rule to write equations for a circuit

## Method — The loop rule

Around any closed loop,  $\sum V = 0$ : the potential rises across the battery equal the drops across the resistors.

## Method — Why it holds

A charge returning to its start has the **same** potential energy, so the total change around the loop is zero — this is conservation of energy.

## Method — Example

A single loop with a 12 V battery and resistors  $R_1$ ,  $R_2$  in series:  $12 = IR_1 + IR_2$ .

## Practice 2.1 ■ 1 mark

State Kirchhoff's loop rule.

## Solution 2.1

Method: The loop rule

### Worked steps

the sum of the potential differences around any closed loop is zero **B1**.

## Practice 2.2 ■ 1 mark

State the conservation law that the loop rule expresses.



## Solution 2.2

### Worked steps

conservation of energy **B1**.

## Practice 2.3 ■ 2 marks

A single loop has a 9.0 V battery and resistors  $2.0\ \Omega$  and  $1.0\ \Omega$  in series. Write the loop equation and find the current.

## Solution 2.3

Method: Example

### Worked steps

$$9.0 = I(2.0 + 1.0) \Rightarrow I = 3.0 \text{ A} \quad \text{M1} \quad \text{A1}.$$

## Exam-style 3.1 ■ 1 mark

Kirchhoff's loop rule states that around a closed loop the sum of the potential differences is

- A** a maximum
- B** zero
- C** equal to the emf only
- D** always negative

## Solution 3.1

Method: The loop rule

A a maximum

B zero



C equal to the emf only

D always negative

### Worked steps

B.

## Exam-style 3.2 ■ 1 mark

The loop rule is a statement of conservation of

**A** charge

**B** energy

**C** momentum

**D** mass

## Solution 3.2

**A** charge

**B** energy



**C** momentum

**D** mass

### Worked steps

**B.**

## Exam-style 3.3 ■ 2 marks

A single loop contains a 6.0 V battery and resistors of  $4.0\ \Omega$  and  $2.0\ \Omega$  in series.

- (a) Write the loop equation.
- (b) Find the current.



## Solution 3.3

Method: Example

### Worked steps

$$(a) \ 6.0 = I(4.0) + I(2.0) \quad \text{M1} \quad \text{A1}. \quad (b) \ I = \frac{6.0}{6.0} = 1.0 \text{ A} \quad \text{B1}.$$