

Exercise walk-through

Capacitors ■ 10.3

eXercise

You must be able to

- define **capacitance** 电容 as $C = \frac{Q}{V}$
- use the parallel-plate result $C = \frac{\epsilon_0 A}{d}$
- calculate the **energy stored**, $U = \frac{1}{2} CV^2 = \frac{1}{2} \frac{Q^2}{C}$
- combine capacitors in **series and parallel** 串联和并联

Method — Capacitance

$C = \frac{Q}{V}$ (farads). For parallel plates, $C = \frac{\epsilon_0 A}{d}$ — larger area or smaller gap gives more capacitance.

Method — Energy stored

$$U = \frac{1}{2} CV^2 = \frac{1}{2} \frac{Q^2}{C}, \text{ stored in the field (energy density } u = \frac{1}{2} \epsilon_0 E^2 \text{)}.$$

Method — Combining capacitors

- **Parallel:** $C = C_1 + C_2 + \dots$
- **Series:** $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$ (less than the smallest).

Practice 2.1 ■ 2 marks

A parallel-plate capacitor has area 0.020 m^2 and separation 1.0 mm ($\epsilon_0 = 8.85 \times 10^{-12}$). Find its capacitance.

Solution 2.1

Method: Capacitance

Worked steps

$$C = \frac{\epsilon_0 A}{d} = \frac{(8.85 \times 10^{-12})(0.020)}{1.0 \times 10^{-3}} = 1.8 \times 10^{-10} \text{ F} \quad \text{M1} \quad \text{A1}.$$

Practice 2.2 ■ 1 mark

Two $4.0\ \mu\text{F}$ capacitors are connected in parallel. Find the total capacitance.

Solution 2.2

Worked steps

$$C = 4.0 + 4.0 = 8.0 \mu\text{F} \quad \text{B1}.$$

Practice 2.3 ■ 2 marks

Find the energy stored in a $10\ \mu\text{F}$ capacitor at $12\ \text{V}$.

Solution 2.3

Method: Energy stored

Worked steps

$$U = \frac{1}{2} CV^2 = \frac{1}{2} (10 \times 10^{-6}) (12)^2 = 7.2 \times 10^{-4} \text{ J} \quad \text{M1} \quad \text{A1}.$$

Exam-style 3.1 ■ 1 mark

The capacitance of a parallel-plate capacitor is

A $\frac{\epsilon_0 d}{A}$

B $\frac{\epsilon_0 A}{d}$

C $\epsilon_0 A d$

D $\frac{A}{\epsilon_0 d}$

Solution 3.1

Method: Capacitance

A $\frac{\epsilon_0 d}{A}$

B $\frac{\epsilon_0 A}{d}$



C $\epsilon_0 A d$

D $\frac{A}{\epsilon_0 d}$

Worked steps

B.

Exam-style 3.2 ■ 1 mark

Two capacitors in series have a total capacitance that is

- A** the sum of the two
- B** less than either one
- C** the larger of the two
- D** zero

Solution 3.2

Method: Combining capacitors

- A the sum of the two
- B less than either one
- C the larger of the two
- D zero



Worked steps

B.

Exam-style 3.3 ■ 2 marks

A $5.0\ \mu\text{F}$ capacitor is charged to $100\ \text{V}$.

- (a) Find the charge stored.
- (b) Find the energy stored.

Solution 3.3

Method: Energy stored

Worked steps

$$(a) \quad Q = CV = (5.0 \times 10^{-6})(100) = 5.0 \times 10^{-4} \text{ C} \quad \text{M1 A1}. \quad (b) \quad U = \frac{1}{2}CV^2 = \frac{1}{2}(5.0 \times 10^{-6})(100)^2 = 0.025 \text{ J} \quad \text{M1 A1}.$$