

Exercise walk-through

Kirchhoff's Loop Rule ■ 11.6

eXercise

You must be able to

- state **Kirchhoff's loop rule** 基尔霍夫电压定律, $\sum \Delta V = 0$ around any closed loop
- explain it as a consequence of **conservation of energy** 能量守恒
- assign consistent **sign conventions** for emf sources and resistors
- write and solve **loop equations**

Method — The loop rule

Around any closed loop, $\sum \Delta V = 0$ — the rises across the emf sources balance the drops across the resistors.

Method — Why it holds

A charge returning to its starting point has the **same** potential energy, so the potential changes around the loop sum to zero (conservation of energy).

Method — Signs

Going around the loop: a resistor traversed with the current is a **drop** ($-IR$); an emf traversed from $-$ to $+$ is a **rise** ($+\varepsilon$).

Practice 2.1 ■ 1 mark

State Kirchhoff's loop rule.

Solution 2.1

Method: The loop rule

Worked steps

the sum of the potential differences around any closed loop is zero **B1**.

Practice 2.2 ■ 1 mark

State the conservation law the loop rule expresses.

Solution 2.2

Worked steps

conservation of energy **B1**.

Practice 2.3 ■ 2 marks

A single loop has a 10 V battery and resistors $2.0\ \Omega$ and $3.0\ \Omega$ in series. Find the current.

Solution 2.3

Worked steps

$$10 = I(2.0 + 3.0) \Rightarrow I = 2.0 \text{ A} \quad \text{M1} \quad \text{A1}.$$

Exam-style 3.1 ■ 1 mark

Kirchhoff's loop rule sums the potential differences around a closed loop to

- A** the emf
- B** zero
- C** a maximum
- D** infinity

Solution 3.1

Method: The loop rule

A the emf

B zero



C a maximum

D infinity

Worked steps

B.

Exam-style 3.2 ■ 1 mark

The loop rule expresses conservation of

A charge

B energy

C momentum

D mass

Solution 3.2

A charge

B energy



C momentum

D mass

Worked steps

B.

Exam-style 3.3 ■ 2 marks

A single loop contains a 12 V battery and resistors of $3.0\ \Omega$ and $1.0\ \Omega$ in series.

- (a) Write the loop equation.
- (b) Find the current.

Solution 3.3

Worked steps

$$(a) \ 12 = I(3.0) + I(1.0) \quad \text{M1} \quad \text{A1}. \quad (b) \ I = \frac{12}{4.0} = 3.0 \text{ A} \quad \text{B1}.$$