

Exercise walk-through

Resistor-Capacitor (RC) Circuits ■ 11.8

eXercise

You must be able to

- describe the **charging** and **discharging** of a capacitor through a resistor
- define the **time constant** 时间常数 $\tau = RC$
- use $q(t) = Q(1 - e^{-t/\tau})$ (charging) and $q(t) = Q e^{-t/\tau}$ (discharging)
- analyse the **initial** and **steady-state** behaviour

Method — Charging and discharging

$$q(t) = Q \left(1 - e^{-t/\tau}\right) \text{ (charging),} \quad q(t) = Q e^{-t/\tau} \text{ (discharging).}$$

Method — Time constant

$\tau = RC$ is the characteristic time; after one τ the charge reaches about 63% (charging) or falls to 37% (discharging).

Method — Start and steady state

At $t = 0$ an uncharged capacitor acts like a **wire** (current $I_0 = V/R$); at steady state it is fully charged and carries **no** current.

Practice 2.1 ■ 2 marks

Find the time constant of a $5.0 \text{ k}\Omega$ resistor and a $20 \text{ }\mu\text{F}$ capacitor.

Solution 2.1

Method: Time constant

Worked steps

$$\tau = RC = (5.0 \times 10^3)(20 \times 10^{-6}) = 0.10 \text{ s} \quad \text{M1} \quad \text{A1}.$$

Practice 2.2 ■ 1 mark

State the current a long time after charging begins.

Solution 2.2

Method: Time constant

Worked steps

zero (the capacitor is fully charged) **B1**.

Practice 2.3 ■ 1 mark

Write the expression for the charge on a **discharging** capacitor.

Solution 2.3

Method: Time constant

Worked steps

$$q(t) = Q e^{-t/\tau} \text{ B1.}$$

Exam-style 3.1 ■ 1 mark

The time constant of an RC circuit is

A R/C

B RC

C $R + C$

D $1/(RC)$

Solution 3.1

Method: Time constant

A R/C

B RC



C $R + C$

D $1/(RC)$

Worked steps

B.

Exam-style 3.2 ■ 1 mark

At $t = 0$, an uncharged capacitor in an RC circuit behaves like a

A break in the circuit

B plain wire

C battery

D resistor of infinite resistance

Solution 3.2

Method: Start and steady state

A break in the circuit

B plain wire 

C battery

D resistor of infinite resistance

Worked steps

B.

Exam-style 3.3 ■ 2 marks

A $2.0\text{ k}\Omega$ resistor charges a $50\text{ }\mu\text{F}$ capacitor from a 10 V supply.

- (a) Find the time constant.
- (b) Find the initial current (at $t = 0$).

Solution 3.3

Worked steps

$$(a) \tau = RC = (2.0 \times 10^3)(50 \times 10^{-6}) = 0.10 \text{ s} \quad \text{M1 A1}. \quad (b) I_0 = \frac{V}{R} = \frac{10}{2.0 \times 10^3} = 5.0 \times 10^{-3} \text{ A} \quad \text{M1 A1}.$$