

# Boolean Logic

IGCSE Computer Science ■ Topic 10

IGCSE Computer Science



## What we will cover

- 1 What is Boolean logic?
- 2 The six logic gates
- 3 Truth tables
- 4 Logic expressions
- 5 Logic circuits
- 6 Recap


1

Gates

---
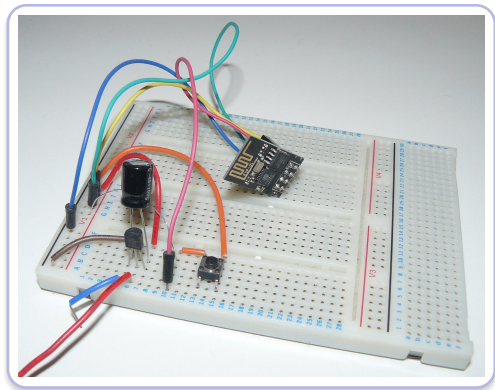
# What is Boolean logic?


**Boolean logic** 布尔逻辑 works with just two values: **TRUE (1)** and **FALSE (0)**. A **logic gate** 逻辑门 takes one or more inputs and gives one output. A **truth table** 真值表 lists the output for **every** combination of inputs.



*Breadboard*
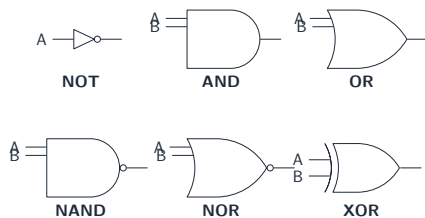
# The six logic gates

- **NOT** – invert
- **AND** – 1 only if all inputs are 1
- **OR** – 1 if any input is 1
- **NAND** / **NOR** – universal (any circuit from these)
- **XOR** – 1 if the inputs differ



*The six logic gates. A small circle on the output means the result is inverted (NOT, NAND, NOR)*

# The six gates, and the rule each one follows

**NOT gate**

One input. The **NOT gate** 非门 *reverses* it: output is 1 when the input is 0.

**AND gate**

Output 1 only when *both* inputs are 1.

**OR gate**

The **OR gate** 或门 gives 1 when *at least one* input is 1.

**NAND gate**

The **NAND gate** 与非门 is AND followed by NOT – the *opposite* of AND.

**NOR gate**


The **NOR gate** 或非门 is OR followed by NOT – the *opposite* of OR.

**XOR gate**

The **XOR gate** 异或门 (exclusive OR) gives 1 when the inputs are *different*.

A small circle on the output means the result is inverted – which is why NOT, NAND and NOR all carry one.

# A real logic chip

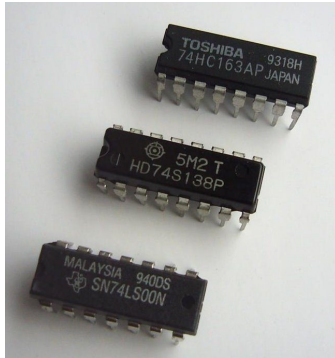

A real logic chip: inside are logic gates like the ones on this page

# Truth tables: AND and OR

| A | B | $A \cdot B$ |
|---|---|-------------|
| 0 | 0 | 0           |
| 0 | 1 | 0           |
| 1 | 0 | 0           |
| 1 | 1 | 1           |

AND

*AND: 1 only when both are 1*

| A | B | $A + B$ |
|---|---|---------|
| 0 | 0 | 0       |
| 0 | 1 | 1       |
| 1 | 0 | 1       |
| 1 | 1 | 1       |

OR

Build a truth table row by row:  
with  $n$  inputs there are  $2^n$  rows – 2  
inputs give 4, 3 inputs give 8. List  
them in binary-counting order so  
you miss none.

## Three inputs give eight rows

**3 inputs**  $\Rightarrow 2 \times 2 \times 2 = 8$  rows

| A | B | C |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |
| 1 | 1 | 1 |

list **every** combination -  
count up in binary,  
from 000 to 111  
the last column flips  
every row, the next  
every two rows,  
the first every four

Three inputs give eight rows: every combination counted in binary

# 2

## Expressions and circuits

---

# Logic expressions

A **logic expression** 逻辑表达式 writes a circuit in words:

$$X = (A \text{ AND } B) \text{ OR } (\text{NOT } C)$$

Work it out **inside the brackets first**, then combine.

Precedence: NOT binds tightest, then AND, then OR. Use brackets to be sure – an examiner reads exactly what you wrote.

# Four ways to say the same logic

**a problem statement**

an alarm (X) sounds when the door is open (A) **AND** the system is switched on (B)

**a logic expression**

$X = A \text{ AND } B$

**a logic circuit**

the gates drawn with their inputs and output

**a truth table**

every input combination and the resulting output

**you must convert**


between **all four**, in either direction

**reading a statement**

pick out the conditions, then the logic words – *and*, *or*, *not*

With  $n$  inputs a truth table has  $2^n$  rows: 2 inputs give 4, 3 inputs give 8. Counting the rows first stops you leaving one out.

The expression  $X = (A \text{ AND } B)$

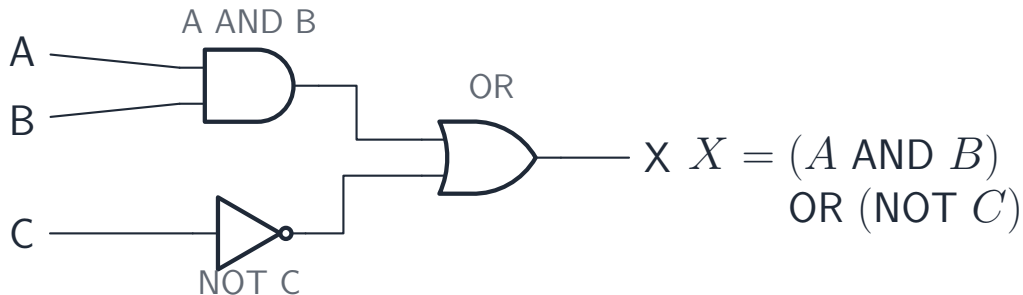

The expression  $X = (A \text{ AND } B) \text{ OR } (\text{NOT } C)$  drawn as a logic circuit


## Worked example – one row of a truth table

**Complete  $X = (A \text{ AND } B) \text{ OR } (\text{NOT } C)$  for the row  $A = 1, B = 0, C = 0$ .**

- work **outwards from the brackets**, one operator at a time
- $A \text{ AND } B = 1 \text{ AND } 0 = 0$
- $\text{NOT } C = \text{NOT } 0 = 1$
- $0 \text{ OR } 1 = 1$

Add a **column per bracket** to the table rather than holding the intermediate values in your head. The marks are for those columns as much as for the answer.

# Logic circuits

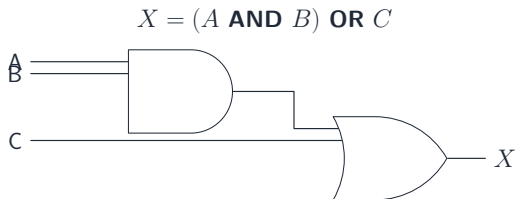

A **logic circuit** 逻辑电路 draws the gates joined by wires. To build its truth table, work **left to right**: find each gate's output, feed it into the next.

Circuit → expression → truth table are three views of the **same** logic – an exam may give you any one and ask for another.

## Exam tips

- Learn all six gates and their truth tables: **NOT**, **AND**, **OR**, **NAND** (NOT AND), **NOR** (NOT OR), **XOR** (output 1 when the inputs are different).
- Build a truth table with *all* input rows (2 inputs  $\rightarrow$  4 rows, 3 inputs  $\rightarrow$  8), counting up in binary, and add a working column for each gate.
- Turn a problem statement into a logic expression by picking out the AND / OR / NOT words, then draw it exactly as written – **do not simplify** it.
- NAND and NOR give the *opposite* output to AND and OR; a small circle on a gate's output means the result is inverted.

3

Recap

---

## Topic 10 – key takeaways

### 1 Two values

TRUE (1) and FALSE (0),  
through gates

### 2 Six gates

NOT, AND, OR, NAND, NOR,  
XOR

### 3 Truth table


$2^n$  rows for  $n$  inputs, in order

### 4 Three views

circuit, expression, table – same  
logic

## Check yourself

- 1 When is an AND gate's output 1?
- 2 How many rows for 3 inputs?
- 3 Which gate outputs 1 when inputs differ?
- 4 Which operator binds tightest?

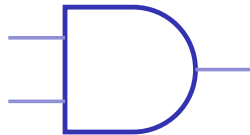

**Answers** 1. when both inputs are 1   2. 8   3. XOR   4. NOT