

Exercise walk-through

Electric circuits ■ 4.3

eXercise

You must be able to


- use the current/p.d. rules for series and parallel circuits
- add series resistors and combine two parallel resistors
- use the potential-divider idea ($\frac{R_1}{R_2} = \frac{V_1}{V_2}$)

Method — Combining resistors


6 Ω and 3 Ω in parallel: $\frac{1}{R} = \frac{1}{6} + \frac{1}{3} = \frac{1}{2} \Rightarrow R = 2 \Omega.$

Method — Combining resistors

series

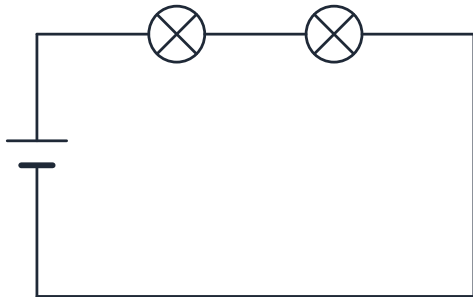


parallel

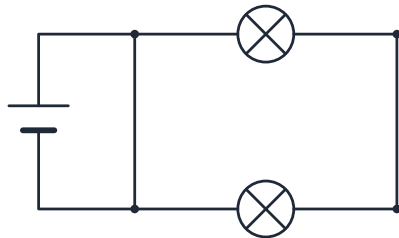

A series circuit (one loop) beside a parallel circuit (separate branches)

Method — Combining resistors

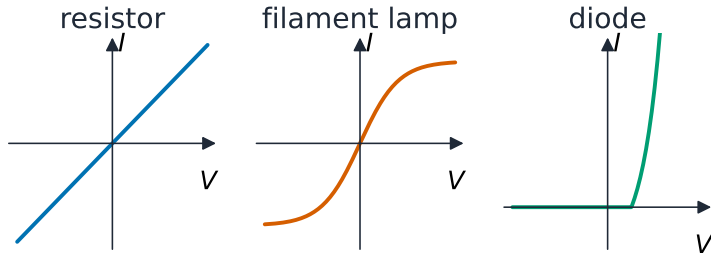

resistor (ohmic): $V = IR$ straight · filament: resistance rises with heat · diode: one-way

I-V graphs: straight line (resistor), S-curve (lamp), one-way (diode)

Practice 2.1 ■ 1 mark

Two resistors of $4\ \Omega$ and $6\ \Omega$ are in series. Find the total resistance.

Solution 2.1

Method: Combining resistors

Worked steps

$$R = 4 + 6 = 10 \, \Omega \quad \text{B1}.$$

Practice 2.2 ■ 1 mark

State how the current behaves at every point in a series circuit.

Solution 2.2

Method: Combining resistors

Worked steps

the current is the same at every point **B1**.

Exam-style 3.1 ■ 1 mark

Compared with the smallest single resistor, two resistors in parallel give a total resistance that is:

- A** larger
- B** smaller
- C** the same
- D** zero

Solution 3.1

Method: Combining resistors

A larger

B smaller



C the same

D zero

Worked steps

B. Two resistors in parallel give a total smaller than the smaller one.

Exam-style 3.2 ■ 3 marks

A 12 V supply is connected to a $4\ \Omega$ and an $8\ \Omega$ resistor in series.

- (a) Find the total resistance and the current.
- (b) Find the p.d. across the $8\ \Omega$ resistor.

Solution 3.2

Method: Combining resistors

Worked steps

$$(a) R = 4 + 8 = 12 \, \Omega \text{ (M1)}; I = \frac{V}{R} = \frac{12}{12} = 1.0 \, \text{A} \text{ (M1) (A1)}.$$

$$(b) V = IR = 1.0 \times 8 = 8.0 \, \text{V} \text{ (M1) (A1)}.$$

Exam-style 3.3 ■ 4 marks

A $6\ \Omega$ and a $12\ \Omega$ resistor are connected in parallel across a $6\ \text{V}$ supply. Find the total resistance and the total current from the supply.

Solution 3.3

Method: Combining resistors

Worked steps

$$\frac{1}{R} = \frac{1}{6} + \frac{1}{12} = \frac{3}{12} = \frac{1}{4} \Rightarrow R = 4 \, \Omega \quad \text{M1 M1}; \quad I = \frac{V}{R} = \frac{6}{4} = 1.5 \, \text{A} \quad \text{M1 A1}.$$